

TESCO METERING

PRACTICAL USE OF VECTORS IN ELECTRIC METERING

Prepared by Perry Lawton, TESCO
TESCO Metering



*North Carolina Meter School
Advanced
Tuesday, June 11, 2024
8:45 AM*

The most basic statement of metering:

Watts = Voltage x Current x Power Factor

Mathematically:

$$Watts = V \times I \times \cos\theta$$

What is a Vector?

A measurement that takes two numbers to represent.

BOTH a magnitude (size) and direction

a Symbolic Representation of the relationship of the voltage and current

- **Vectors & Vector Diagrams**
 - **SIMPLE.** Used to Represent Electrical Quantities.
 - **QUICK.** Saves time.
 - **Vastly more effective**
 - **Also referred to as “Phasors”**

- **Vectors all have MAGNITUDE and DIRECTION**
- **Line length can represent MAGNITUDE.**
- **Line with arrowhead in a given direction indicates that quantity's relationship to any other quantity being represented.**
- **DIRECTION: Angles between lines take on significance. They represent time (shown in degrees instead of seconds).**


General Guidelines

- Complete circle (360 Degrees) equal one cycle of the frequency displayed.
- **One component (Usually Phase A voltage) becomes the reference and is placed at zero degrees.**
- Use “open” arrowhead on voltage line(s).
- Use “closed” (or filled in) arrowhead on current line(s).
- Label all voltages and currents by phase.
- Indicate Phase Rotation (counter-clockwise assumed if not noted).



TESCO METERING

"TIME" IN DEGREES


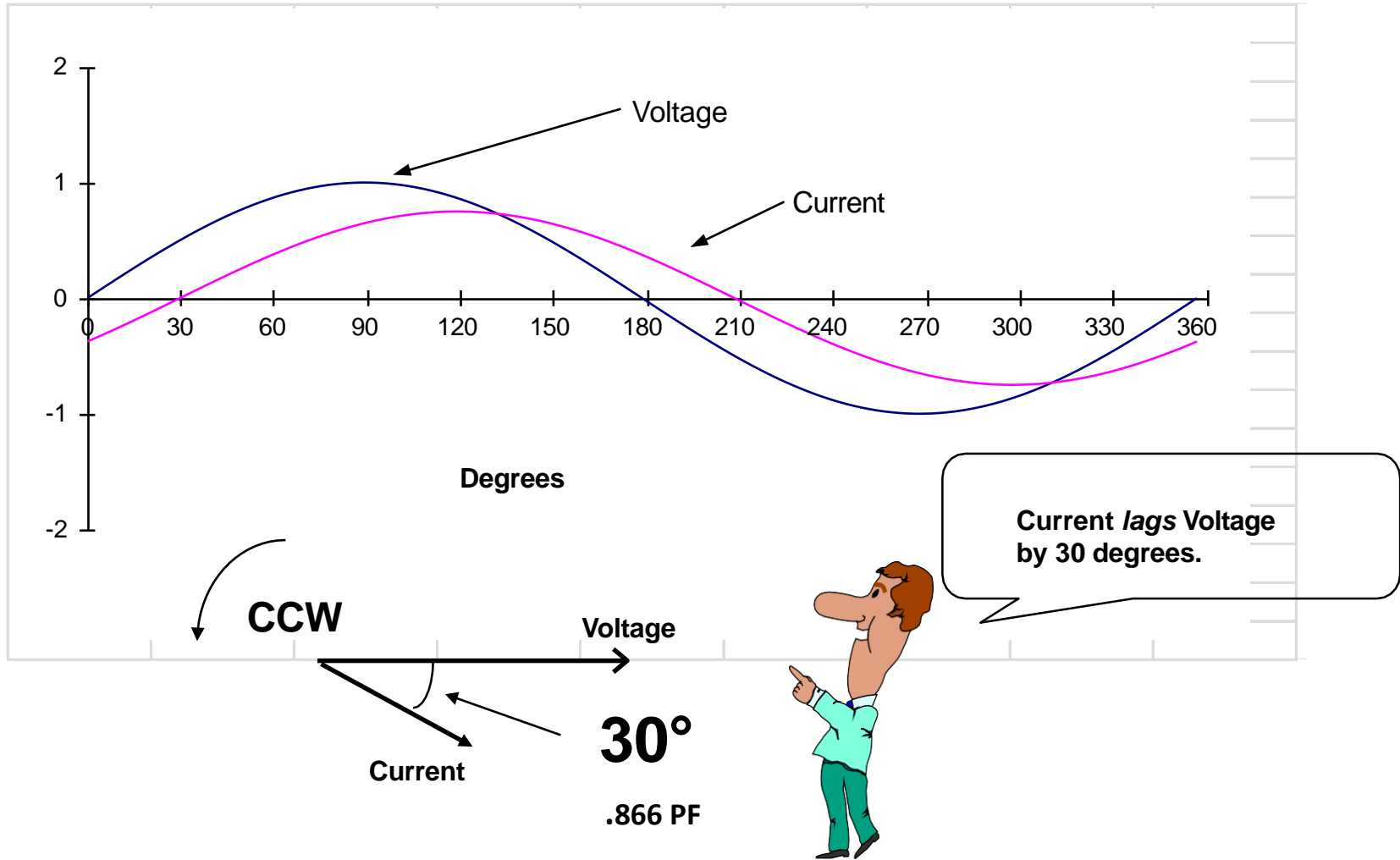




TESCO METERING


"TIME" IN DEGREES

1

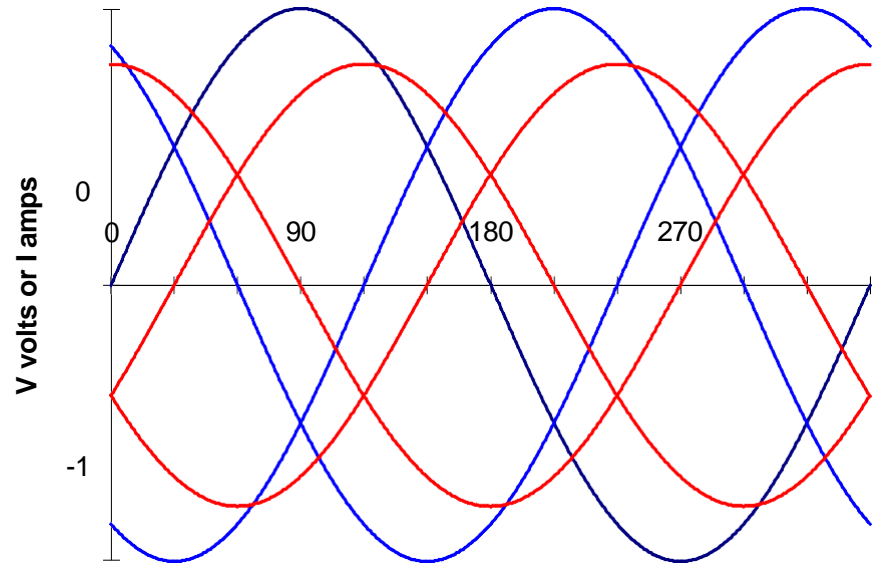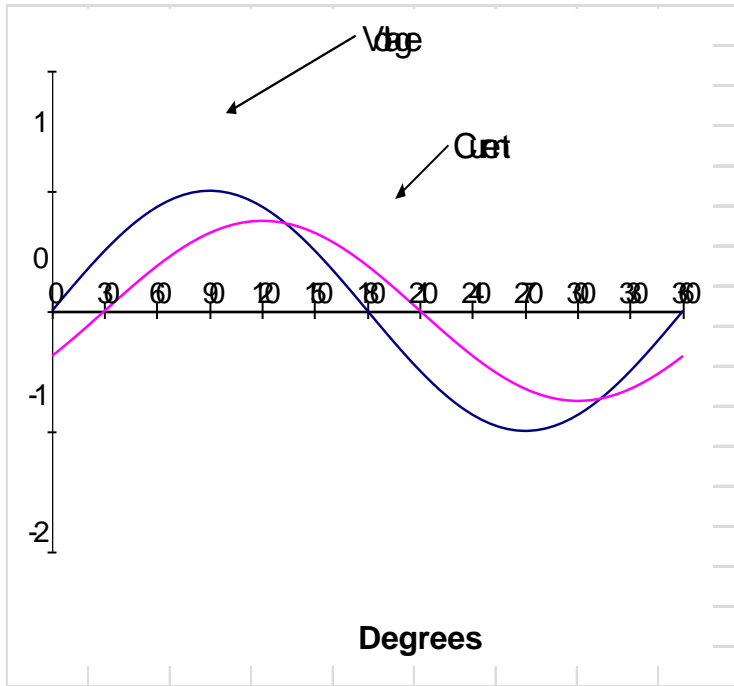


V volts or I amps

Phase Angle (Degrees)

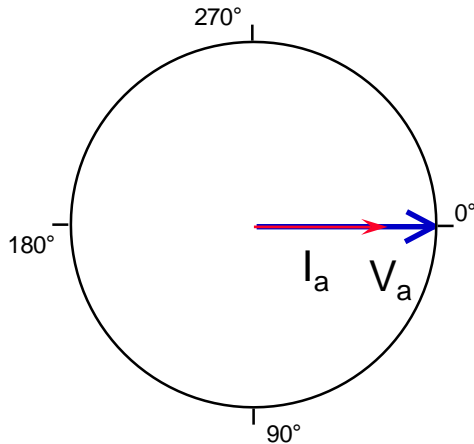

1 Element

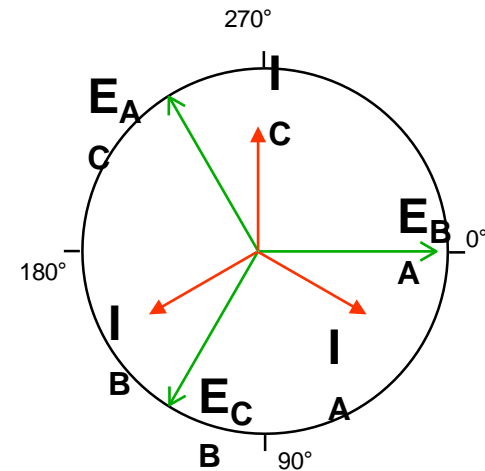


tescometering.com

- **Watthour meter theory review:**
 - If we apply “V” volts and “I” amps to a meter, and the phase angle between the voltage and current is some angle θ , the meter speed will be proportional to:


$$\text{Watts} = V \times I \times \cos\theta$$

VECTORIALLY

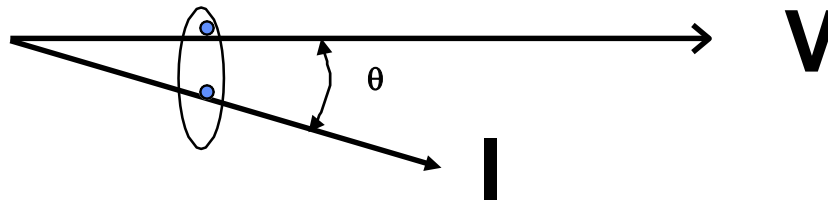


EXPECTED METER PHASORS

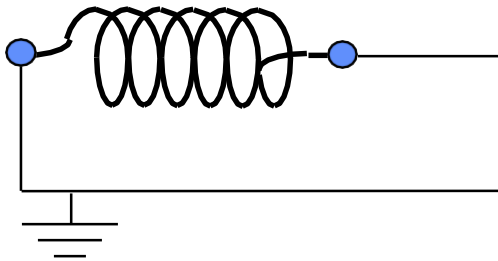
(at Power Factor = 1, ABC Phase Sequence)




2 wire, 1 ϕ

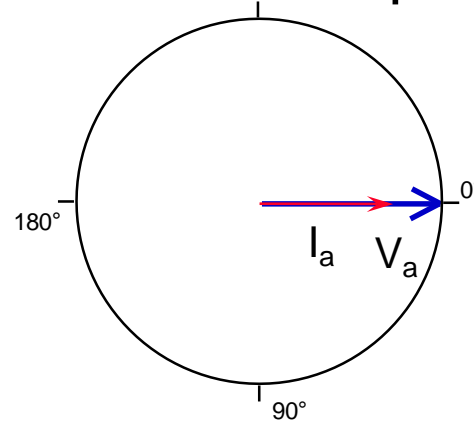


1 Element

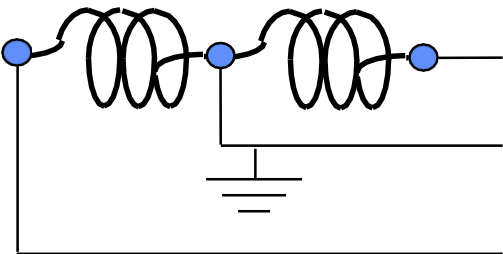


3 wire, 1 ϕ

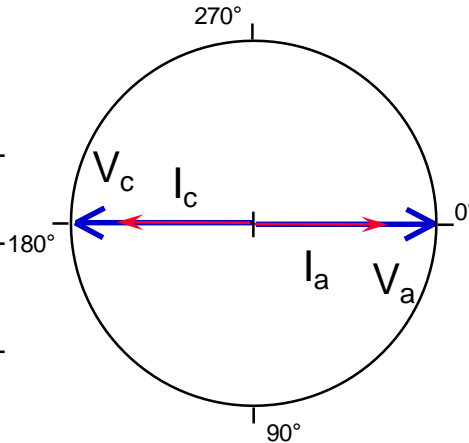

2 Element


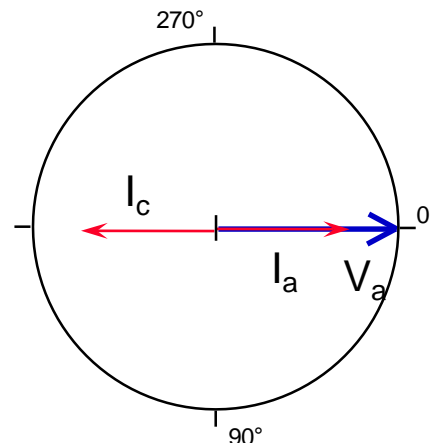


1½ Element

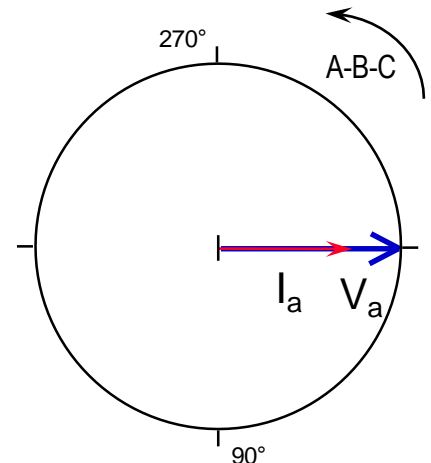

1 Element

PLACING COILS IN ORDER

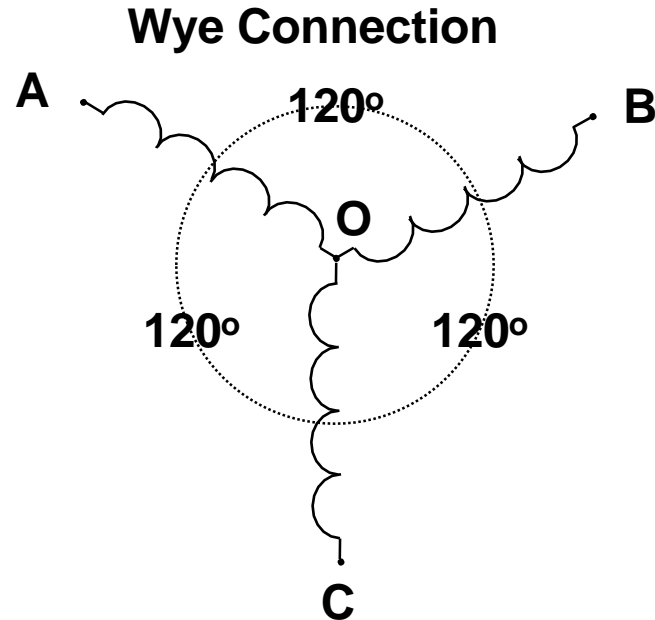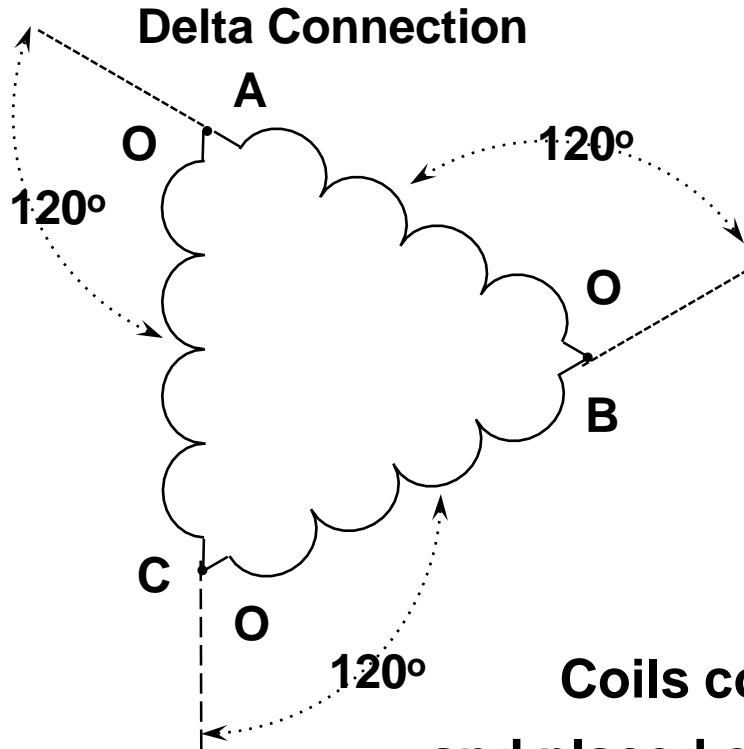

**Coils connected together
and placed on an alternator in order**


OA, OB, and OC

(Changing Coil order changes Sequence)




- A phasor diagram is a method of expressing the magnitudes and time relationships (or phase angle relationships) between two or more sinusoidal quantities of the same frequency.
- Each alternating quantity having the same frequency can be represented on the same diagram by additional lines. Their time relationship will determine the angle between the lines.
- The phasor diagram is a “snap-shot” of the set of lines at an instant in time. The instant is generally chosen to be the time at which the voltage passes through zero in the positive direction. If there is more than one voltage, the instant at which phase A voltage passes through zero is chosen.

REPRESENTING POLYPHASE V & I

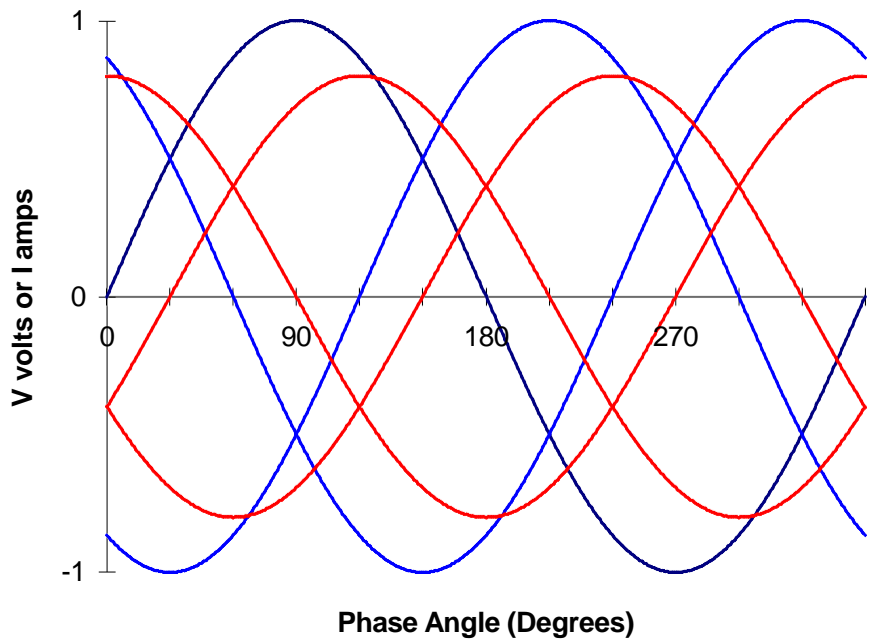

Time Domain Representation

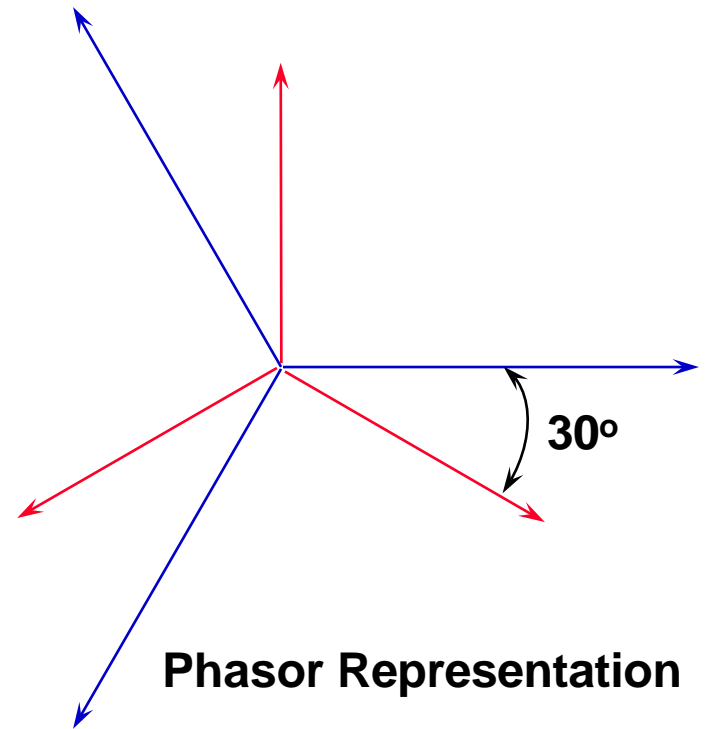

Phasor Representation



TESCO METERING

REPRESENTING *E* & *I* WITH LINES


- **Line length can represent MAGNITUDE.**
- **Line with arrowhead in a given direction indicates that quantity's relationship to any other quantity being represented.**
- **Angles between lines take on significance. They represent time (shown in degrees instead of seconds).**




General Guidelines

- Complete circle (360 Degrees) equal one cycle of the frequency displayed.
- **One component (Usually Phase A voltage) becomes the reference and is placed at zero degrees.**
- Use “open” arrowhead on voltage line(s).
- Use “closed” (or filled in) arrowhead on current line(s).
- Label all voltages and currents by phase.
- Indicate Phase Rotation (counter-clockwise assumed if not noted).

- **Both voltage & current are required in each meter element (stator) for that element to have an effect on registration.**
- **Time relationship (degrees separation) between voltage & current acting together on each element will determine that element's effect.**
- **Only angles of less than 90 Degrees between the current and voltage on any meter element will cause positive watt-hour registration.**

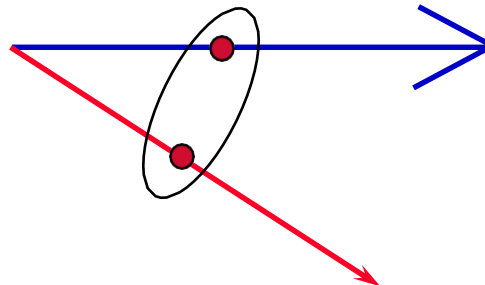


THE PHASOR DIAGRAM

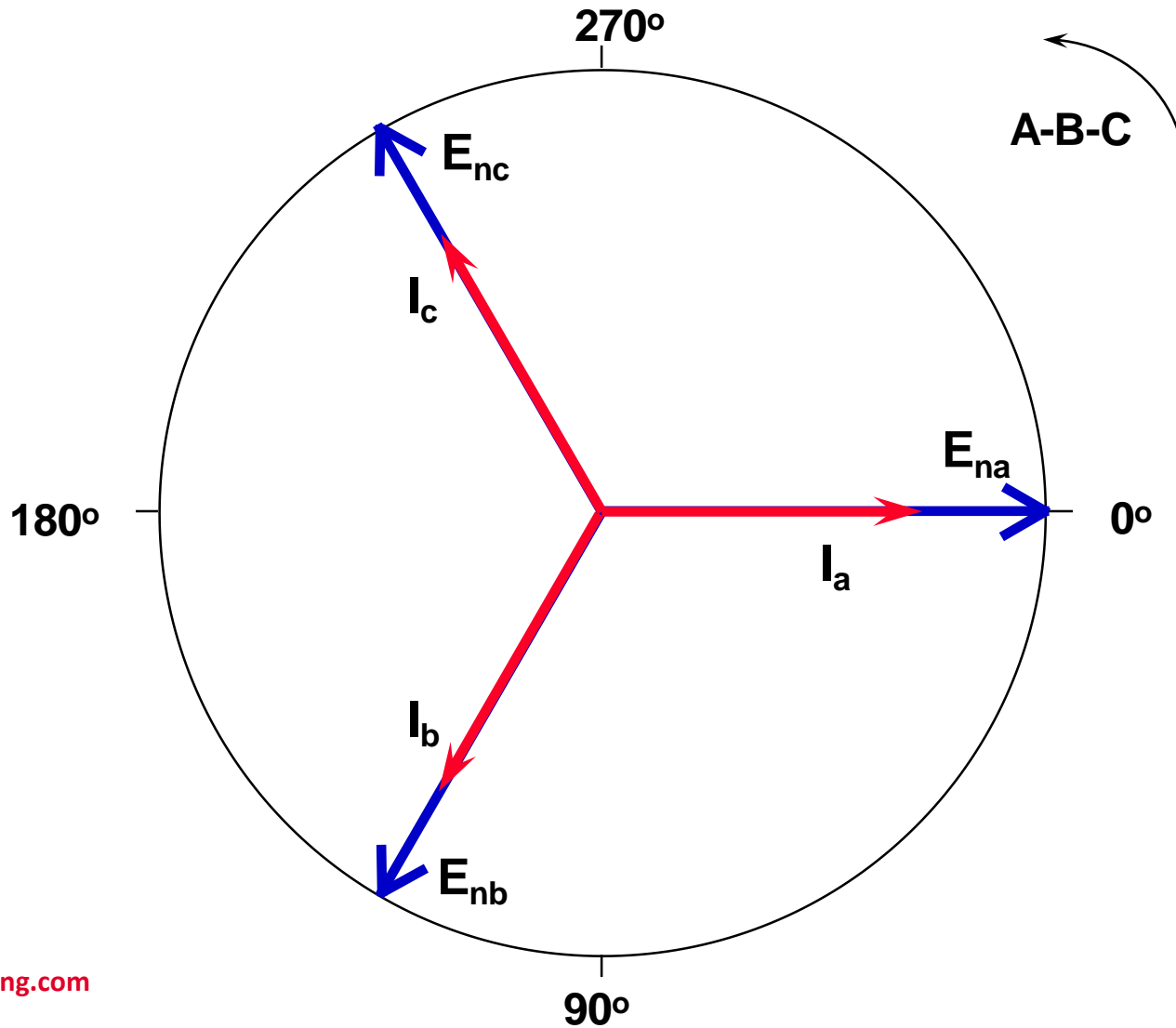




TESCO METERING

SERVICE & METER PHASORS

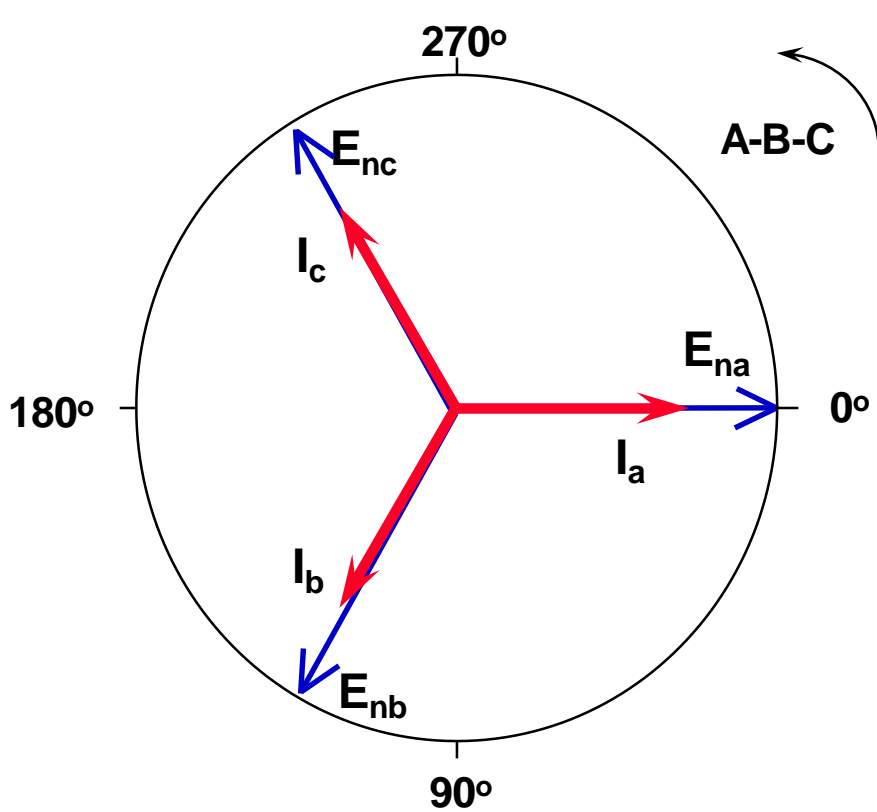

Service Phasors

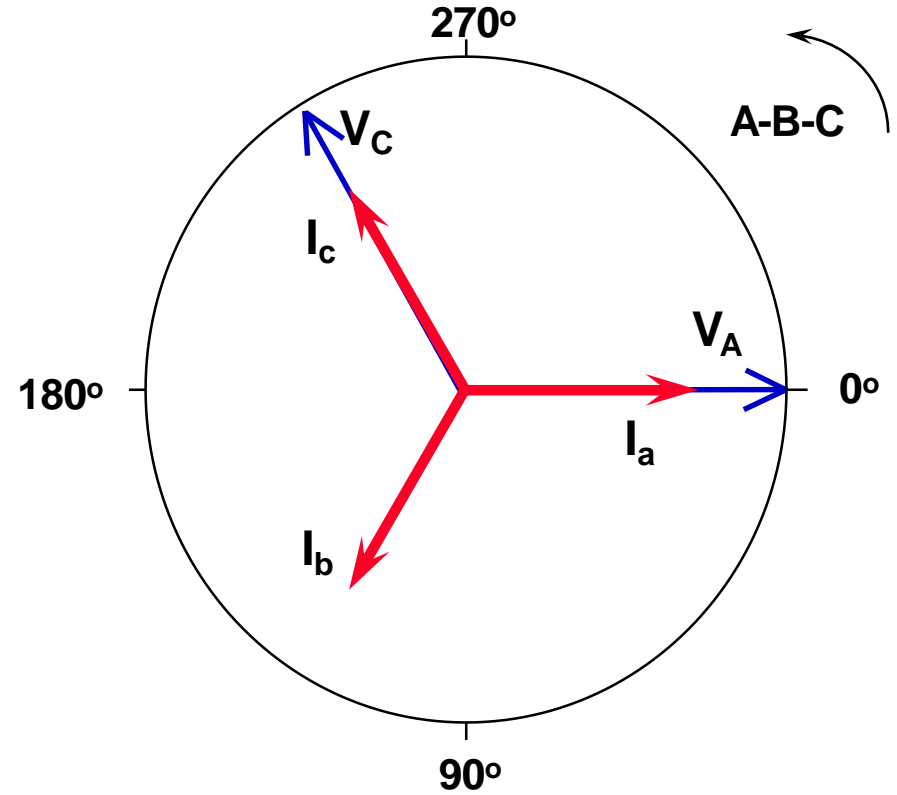

Meter Phasors

2 1/2 Element




TESCO METERING

PHASE ROTATION & SITE MEASUREMENTS


Site Measurements

| Phase | Voltage | Voltage Phase | Current | Current Phase | Probe Current | Probe Phase |
|-------|---------|---------------|---------|---------------|---------------|-------------|
| A | 113.605 | 0.000° | 2.901 | 14.345° | 578.355 | 14.45° |
| B | 114.364 | 120.147° | 3.002 | 136.931° | 599.459 | 137.140° |
| C | 113.611 | 240.312° | 2.864 | 256.188° | 570.920 | 256.198° |

Secondary Phasor

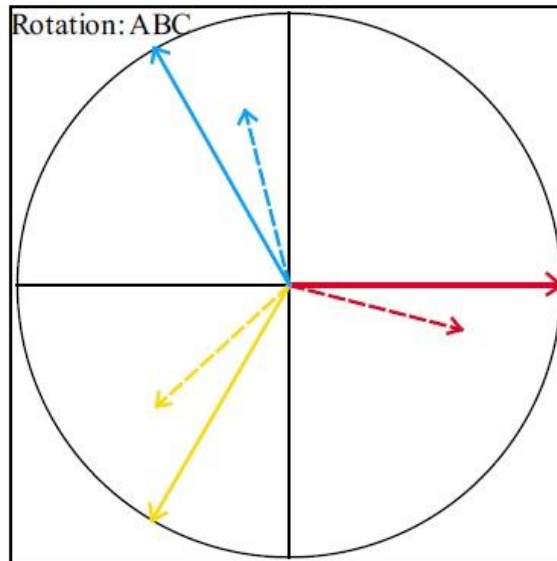









Primary Phasor

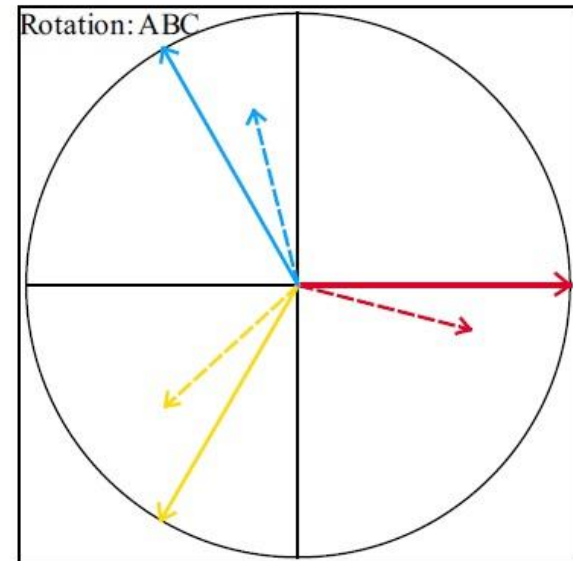


Power

| Phase | Watts | VA | VAR | Voltage THD | Current THD | Power Factor | CT Ratio |
|-------|-------|-------|-------|-------------|-------------|--------------|----------|
| A | 0.354 | 1.464 | 0.360 | 0.016 | 0.075 | 0.966 | 996.98:5 |
| B | 1.456 | 1.525 | 0.438 | 0.016 | 0.073 | 0.955 | 998.58:5 |
| C | 1.387 | 1.445 | 0.393 | 0.016 | 0.075 | 0.959 | 996.57:5 |


LOAD CAUSED PHASE ANGLES

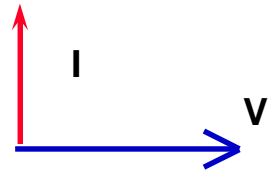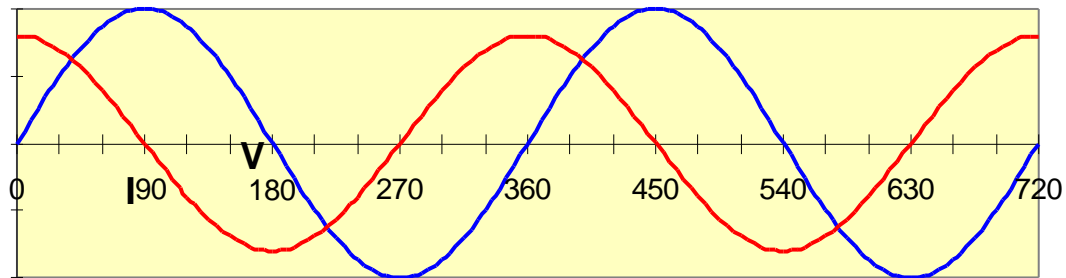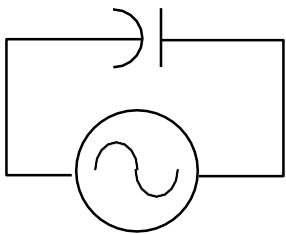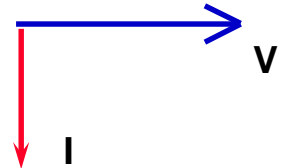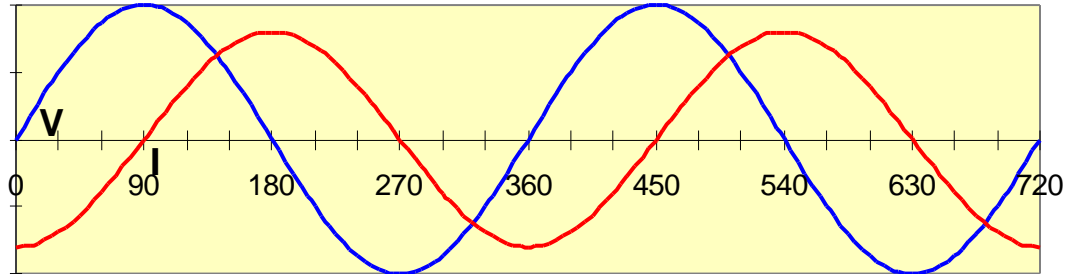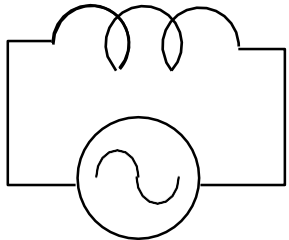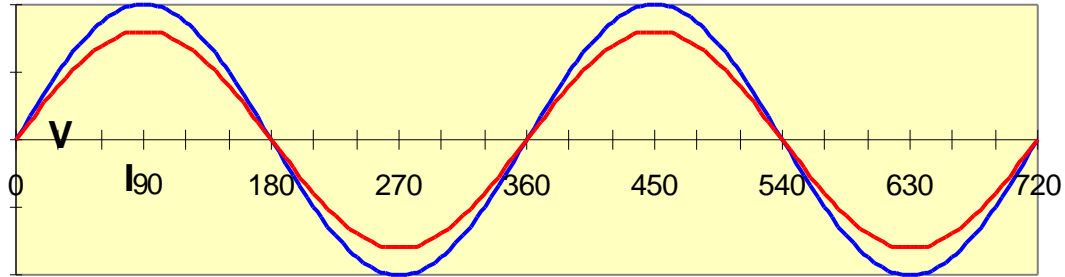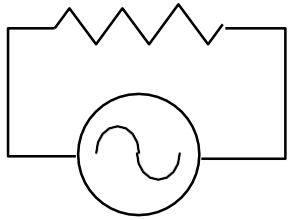

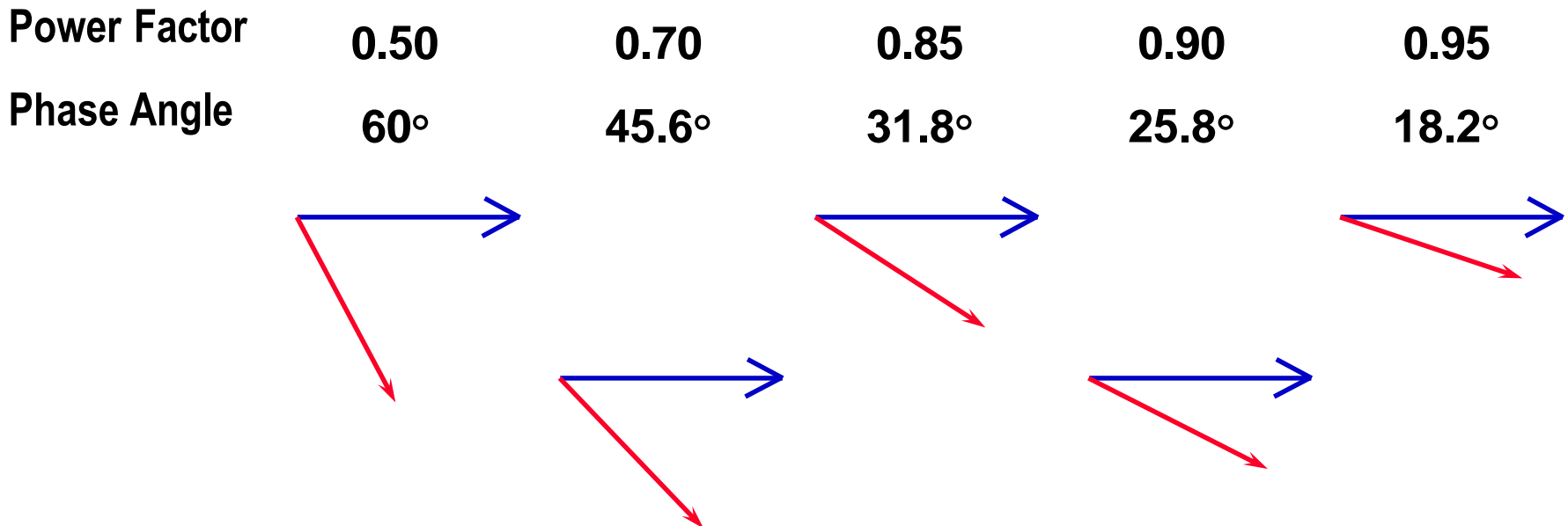- We represent energy as: $Energy = E \times I \times \cos \theta \times t$
 - θ is the angle between V and I
 - $\cos \theta$ is also known as Power Factor
- What θ values give with these lagging Power Factors?




THREE WIRE DELTA SOURCE

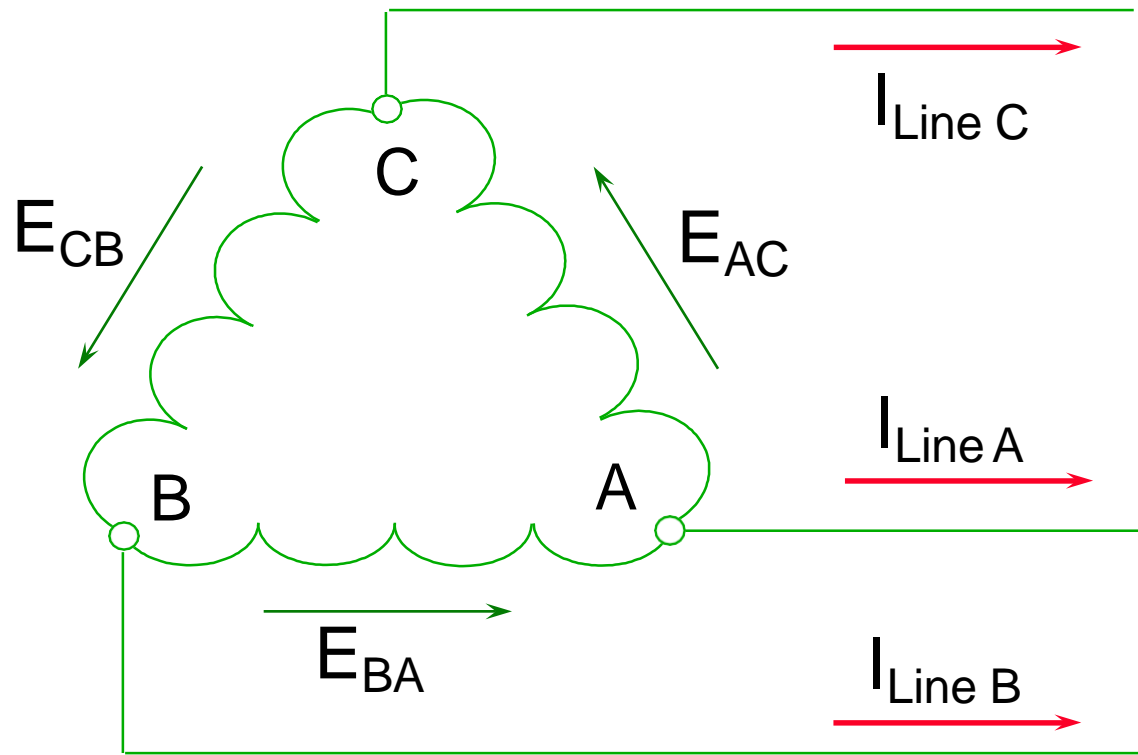

With pure resistance balanced three-phase load, the current in each supply transformer is in phase with the voltage across each transformer.


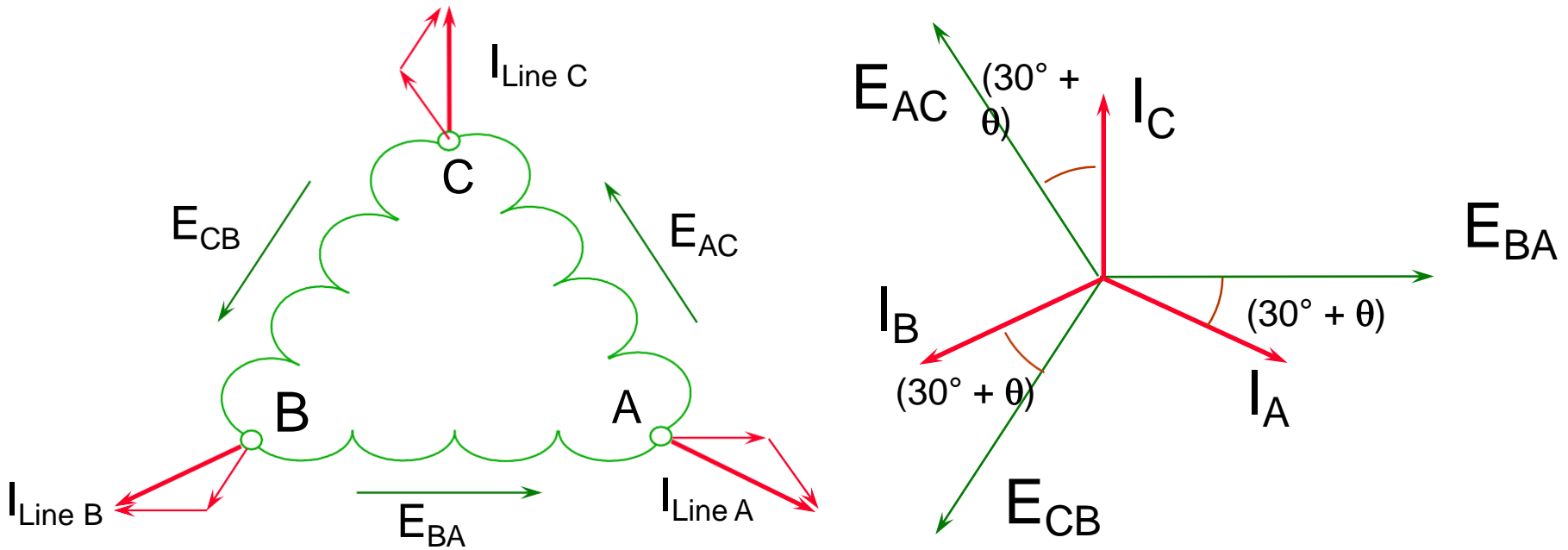
Phasor diagram for delta-connected three-phase system with three-phase delta-connected resistance load




Phase voltages = E_{BA} , E_{CB} , & E_{AC}

Line currents = I_A , I_B , & I_C

PHASORS FOR SOURCE & METER

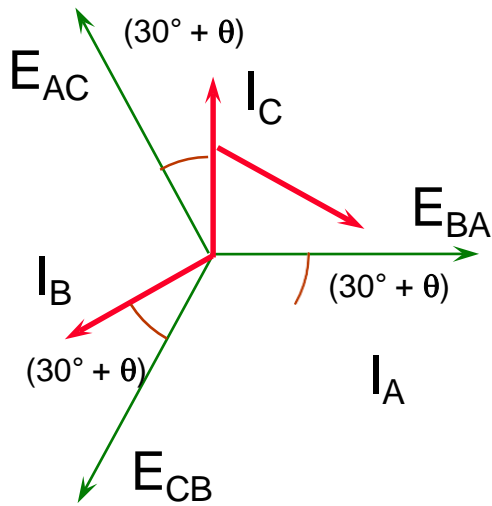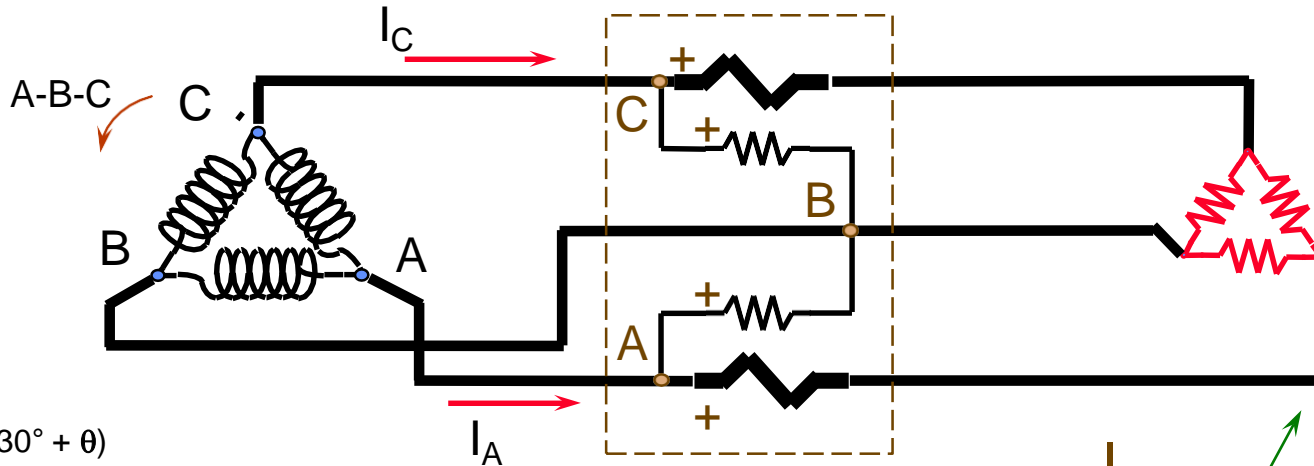


Source

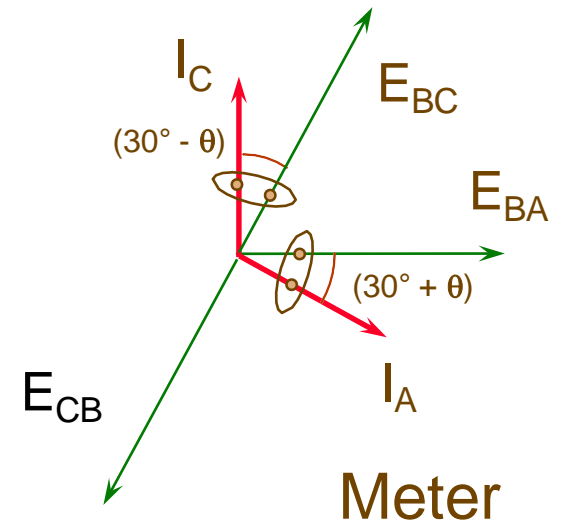


Meter

PHASE SEQUENCE CBA

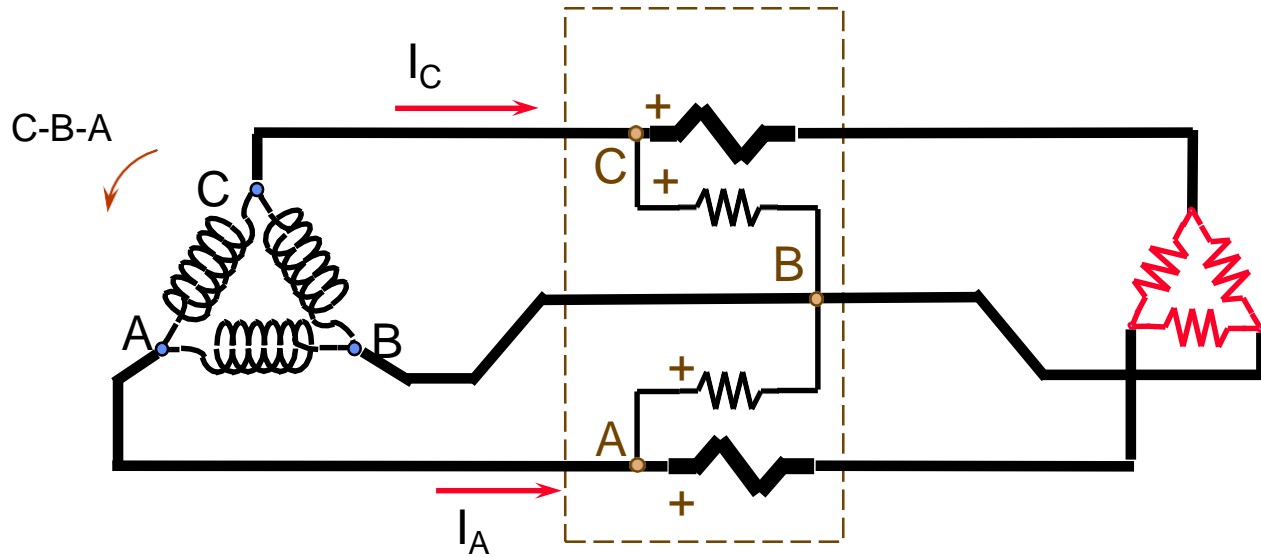


C-B-A
Meter
Phasors

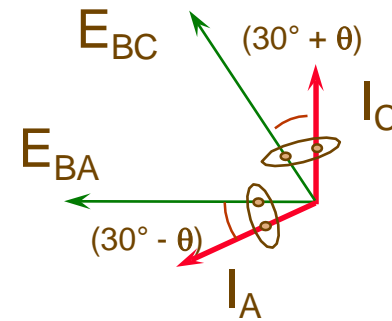




TESCO METERING


COMMON DISTRIBUTION CIRCUITS

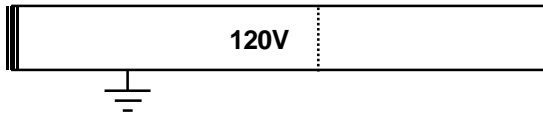


**Two-Wire
Single Phase**

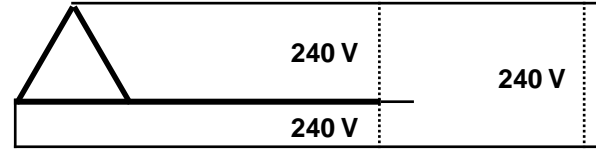


**Three-Wire
Three Phase
Delta**

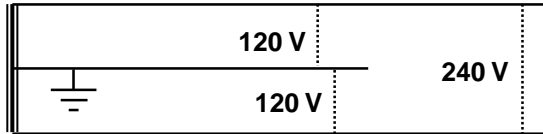


**Three-Wire
Single Phase**

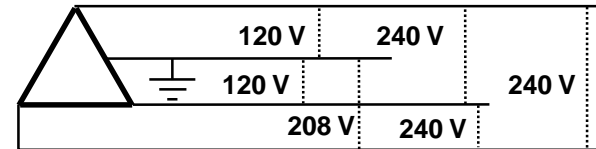

**Four-Wire
Three Phase
Delta**

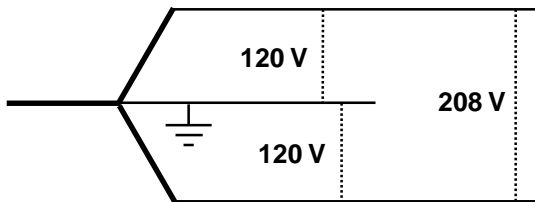

**Three-Wire
Network**

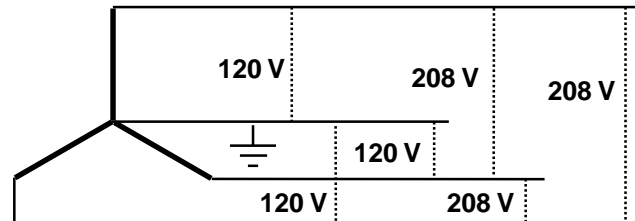


**Four-Wire
Three Phase
Wye**




TESCO METERING

3 ELEMENT EXPECTED METER PHASORS

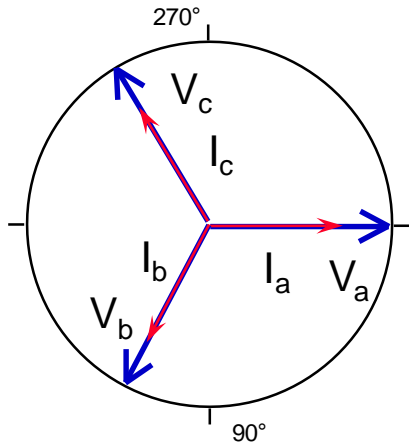
(AT POWER FACTOR = 1, ABC PHASE SEQUENCE)




Balanced Polyphase Load

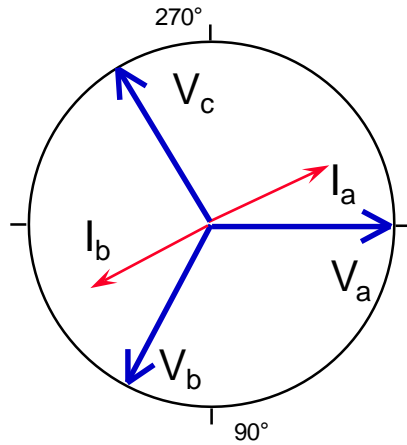


Single phase Load Connected A to B

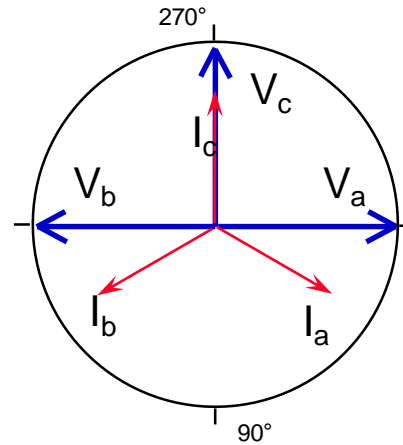


Balanced Polyphase Load

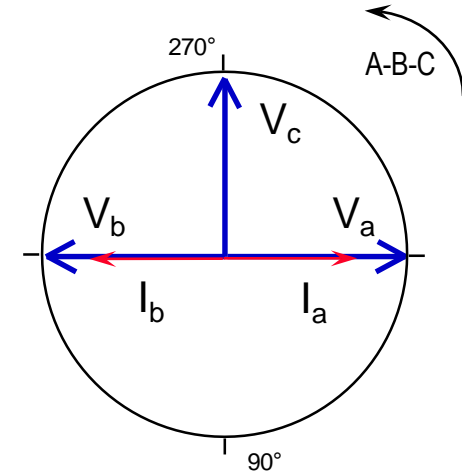

Single phase Load Connected A to B

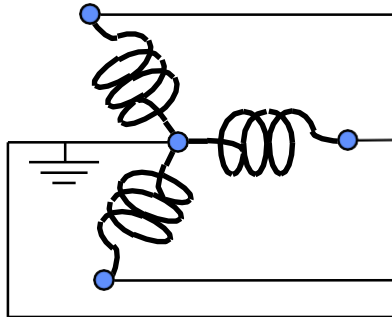






4 wire, wye

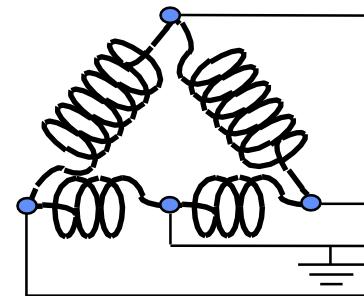


4 wire, delta

2 ELEMENT EXPECTED METER PHASORS

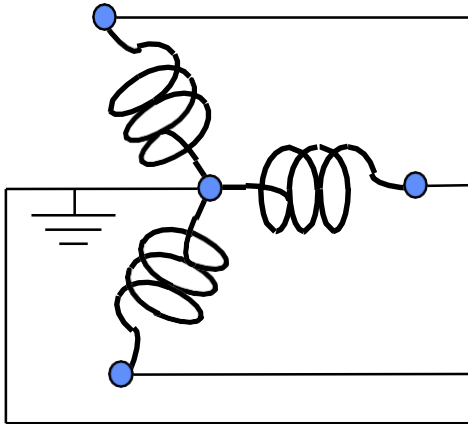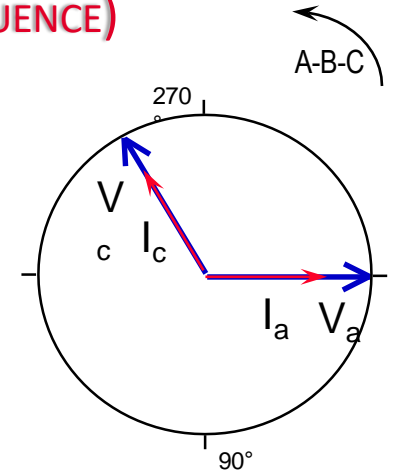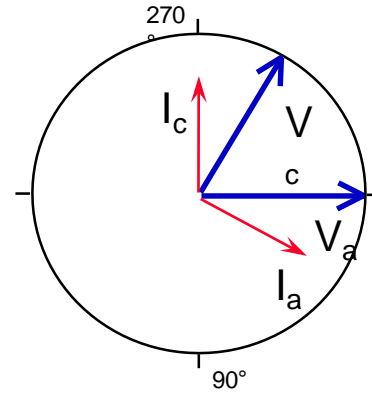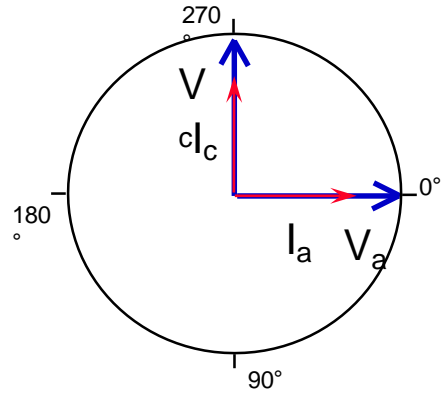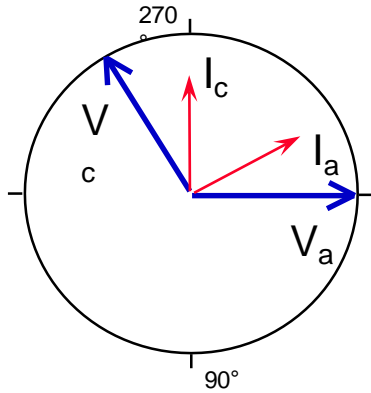
(BALANCED LOAD AT POWER FACTOR = 1, ABC PHASE SEQUENCE)




4 wire, wye

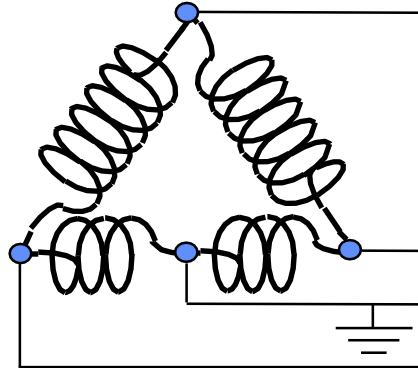

4 wire, delta

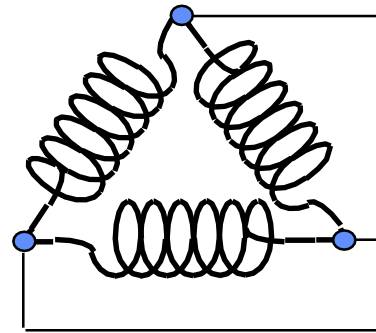

3 wire, delta

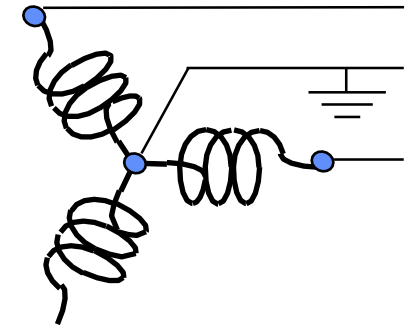



3 wire, network



TESCO METERING


1φ EXPECTED METER PHASORS

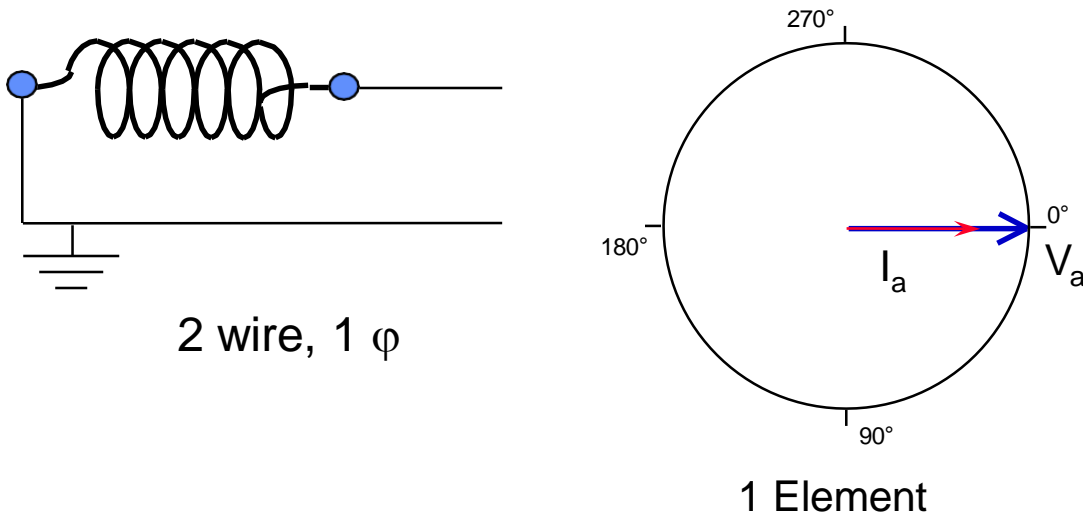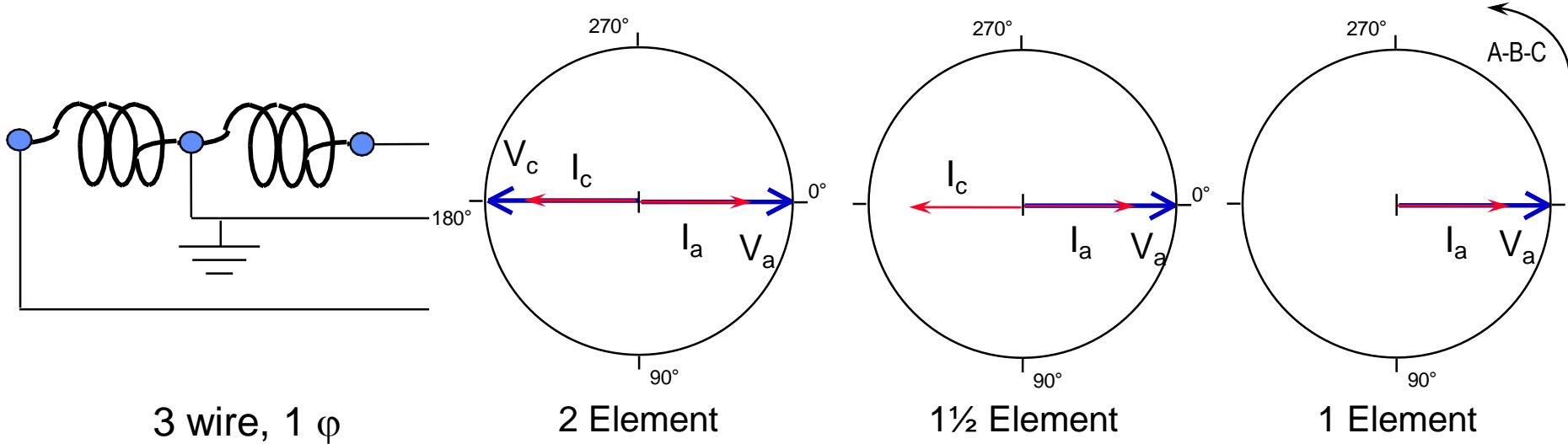(BALANCED LOAD AT POWER FACTOR = 1, ABC PHASE SEQUENCE)




EXPECTED METER PHASORS

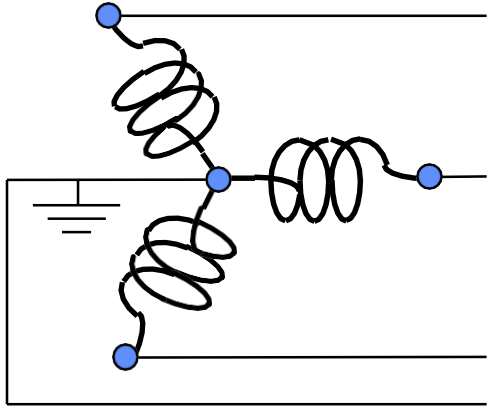
(AT POWER FACTOR = 1, ABC PHASE SEQUENCE)




4 wire, wye

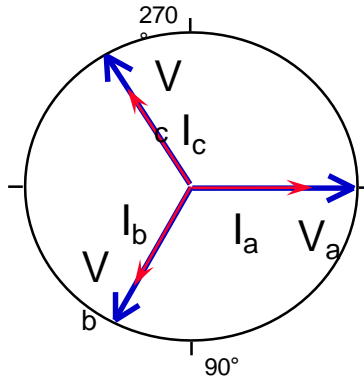


3 Element

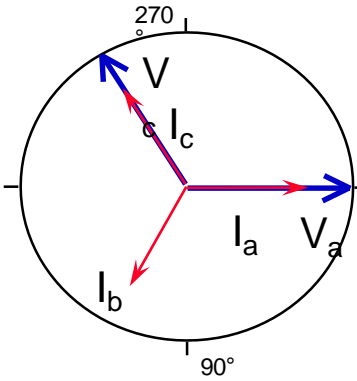


2½ Element

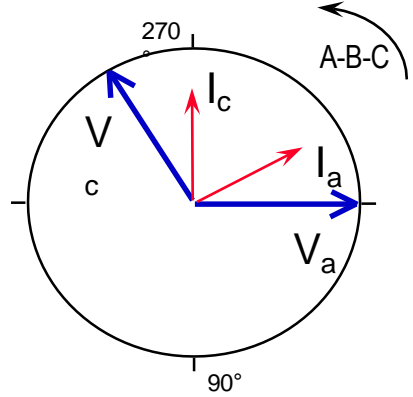


2 Element

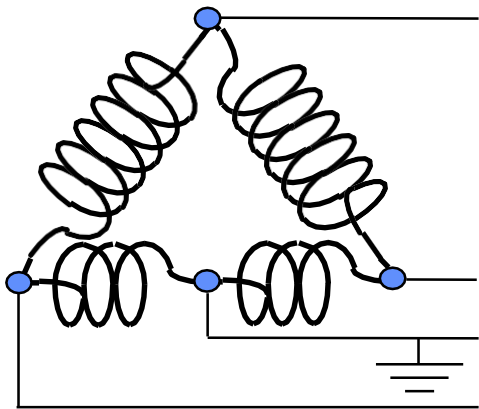

4 wire, delta

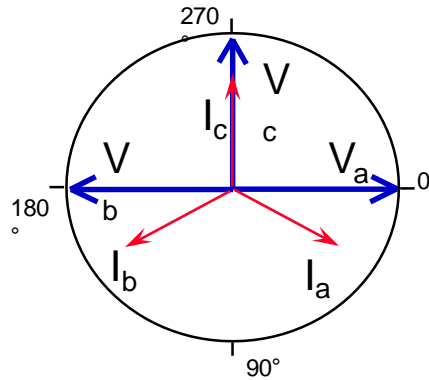


3 Element

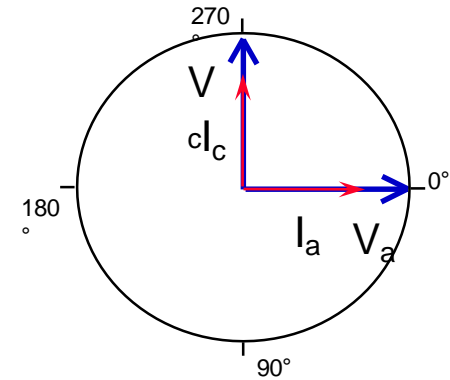


2 Element

EXPECTED METER PHASORS

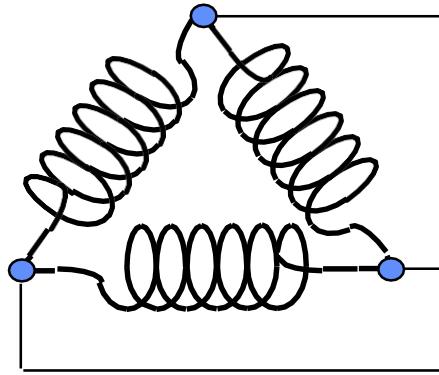
(AT POWER FACTOR = 1, ABC PHASE SEQUENCE)




3 wire, delta

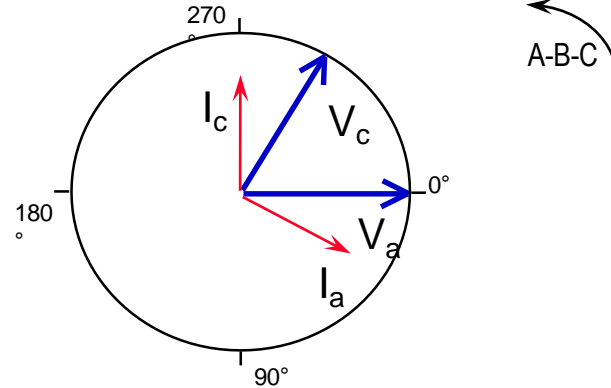

2 Element

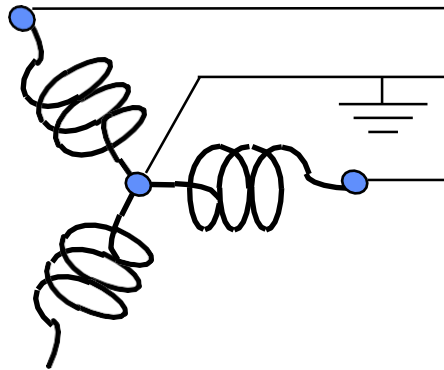


3 wire, network

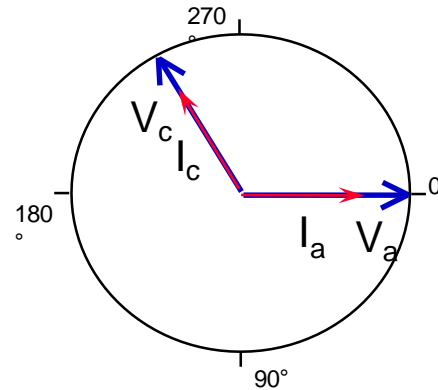

2 Element

EXPECTED METER PHASORS

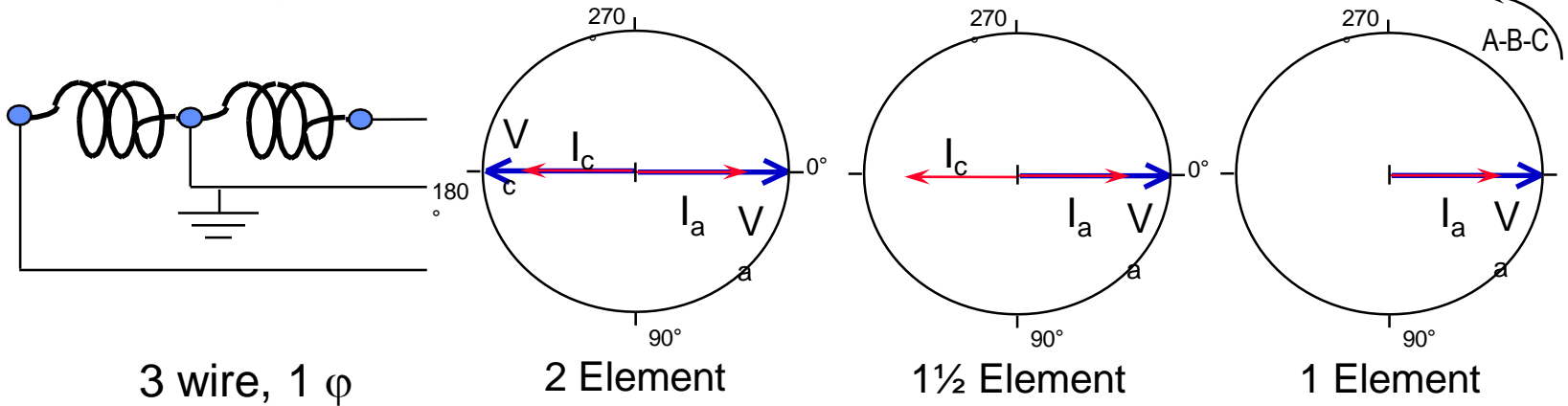(AT POWER FACTOR = 1, ABC PHASE SEQUENCE)






TESCO METERING

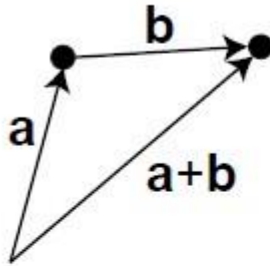Let's Talk about Why We Need to Understand Vectors.






Addition of vectors can be expressed by a diagram. Placing the vectors end to end, the vector from the start of the first vector to the end of the second vector is the sum of the vectors. One way to think of this is that we start at the beginning of the first vector, travel along that vector to its end, and then travel from the start of the second vector to its end. An arrow constructed between the starting and ending points defines a new vector, which is the sum of the original vectors. Algebraically, this is equivalent to adding corresponding terms of the two vectors:


$$\mathbf{a} + \mathbf{b} = \begin{bmatrix} a_x \\ a_y \end{bmatrix} + \begin{bmatrix} b_x \\ b_y \end{bmatrix} = \begin{bmatrix} a_x + b_x \\ a_y + b_y \end{bmatrix}.$$

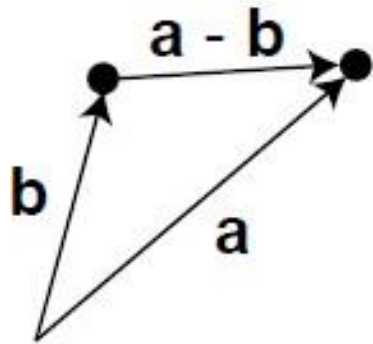We can think of this as again making a trip from the start of the first vector to the end of the second vector, but this time traveling first horizontally the distance $a_x + b_x$ and then vertically the distance $a_y + b_y$.




Subtraction of vectors can be shown in diagram form by placing the starting points of the two vectors together, and then constructing an arrow from the head of the second vector in the subtraction to the head of the first vector. Algebraically, we subtract corresponding terms:
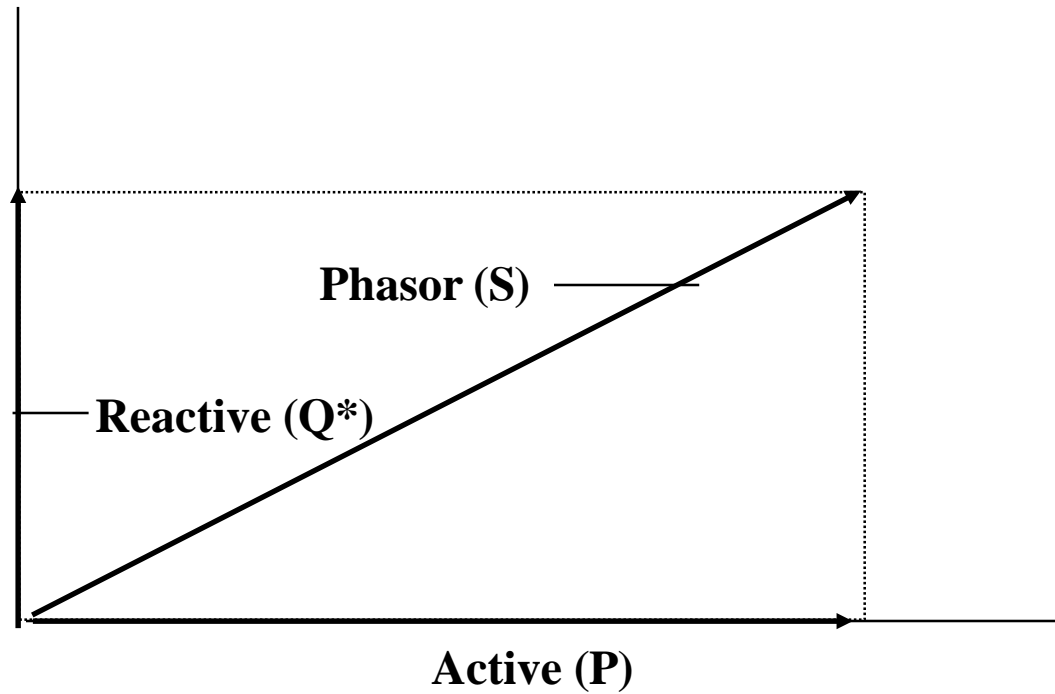
$$\mathbf{a} - \mathbf{b} = \begin{bmatrix} a_x \\ a_y \end{bmatrix} - \begin{bmatrix} b_x \\ b_y \end{bmatrix} = \begin{bmatrix} a_x - b_x \\ a_y - b_y \end{bmatrix}.$$




***Not the “Q” of Q-hour metering**

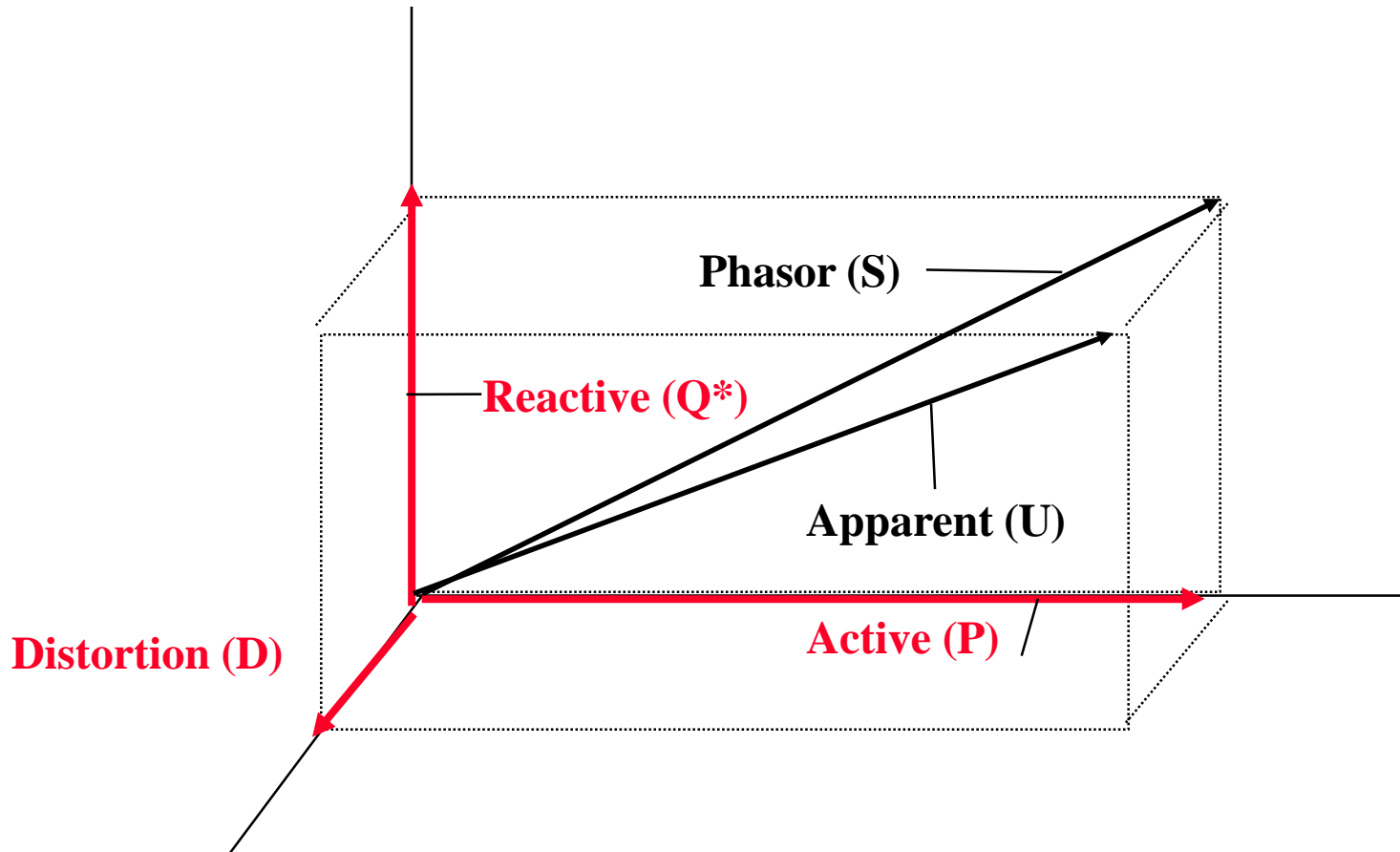

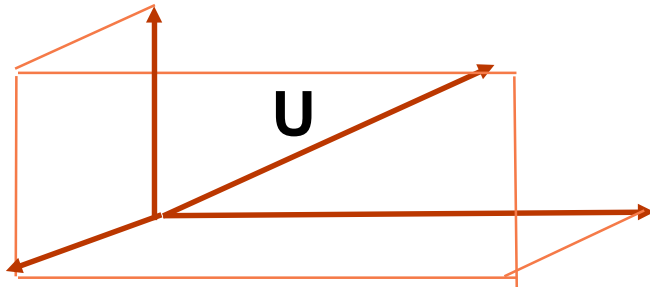***Not the “Q” of Q-hour metering**


HOW IS 3 ϕ APPARENT POWER CALCULATED?

- To calculate Apparent power (U), first add the components for the phases together,




HOW IS 3 ϕ APPARENT POWER CALCULATED?

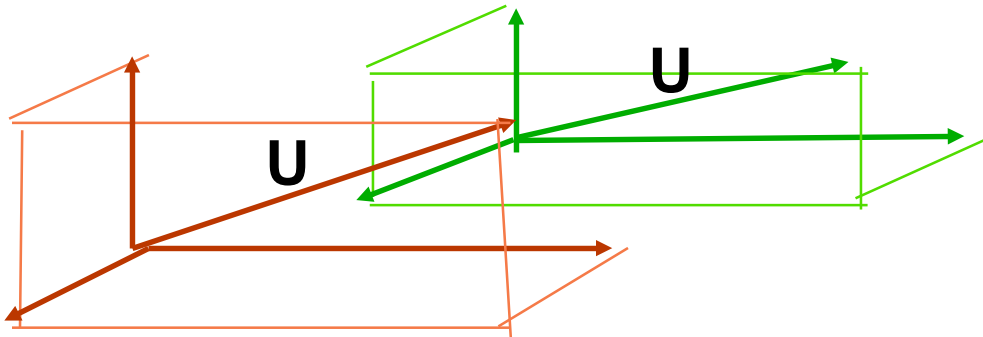- To calculate Apparent power (U), first add the components for the phases together,



HOW IS 3 ϕ APPARENT POWER CALCULATED?

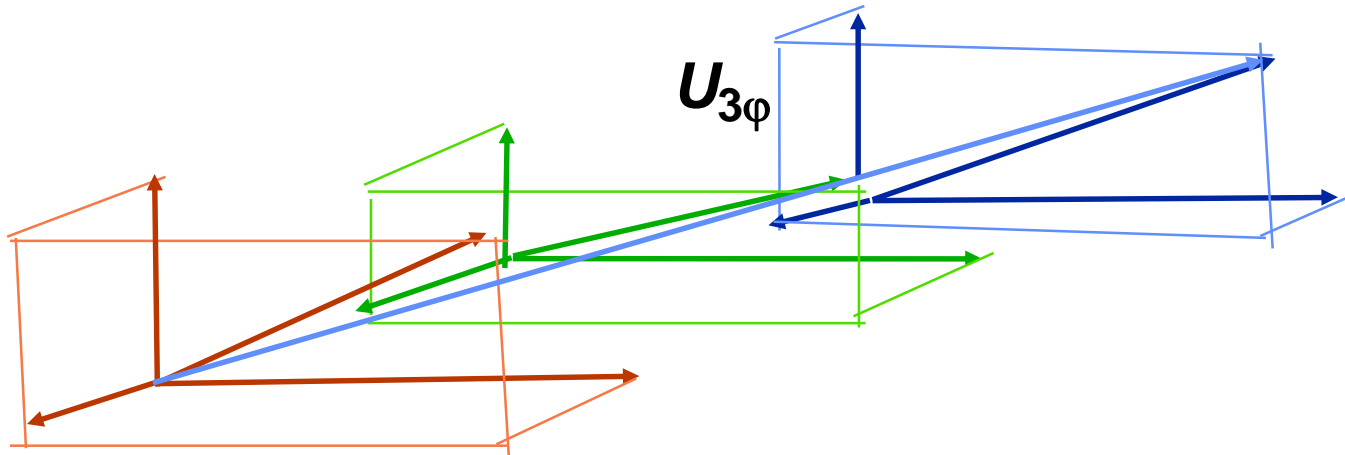- To calculate Apparent power (U), first add the components for the phases together, then solve for U.



$$U_{3\phi} = \sqrt{(P_A + P_B + P_C)^2 + (Q_A + Q_B + Q_C)^2 + (D_A + D_B + D_C)^2}$$

$$S = \sqrt{(P_A + P_B + P_C)^2 + (Q_A + Q_B + Q_C)^2}$$


$$U_{(\text{arith})} = U_A + U_B + U_C$$



APPARENT POWER VS. ARITHMETIC APPARENT POWER

- To calculate Apparent power (U), first add the components for the phases together, then solve for U .
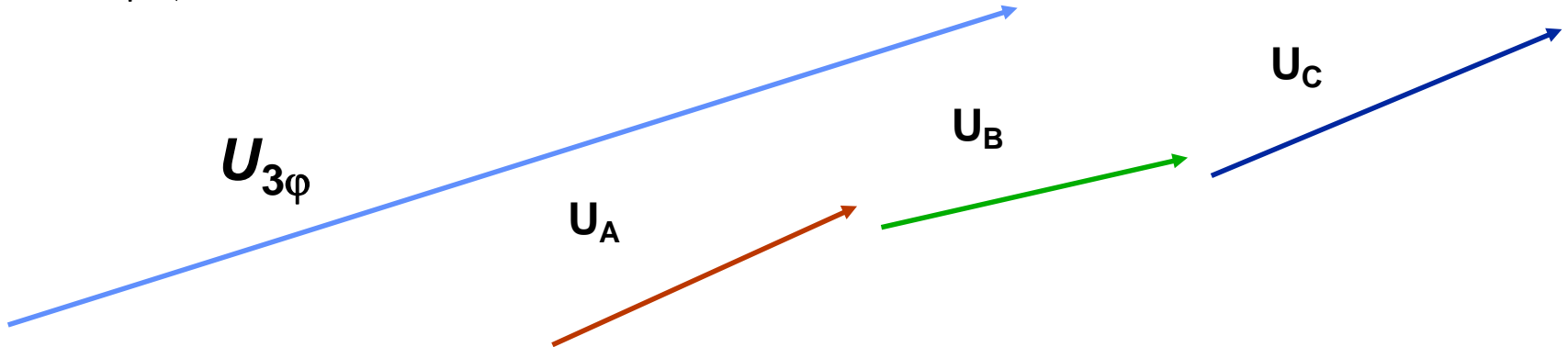
$$U_{3\phi} = \sqrt{(P_A + P_B + P_C)^2 + (Q_A + Q_B + Q_C)^2 + (D_A + D_B + D_C)^2}$$



- To calculate *Arithmetic* Apparent power, add the Apparent power magnitudes of the three individual phases.

$$U_{Arithmetic} = U_A + U_B + U_C$$



TESCO METERING

ALL KVAS ARE NOT CREATED EQUAL

| Power Calculations | | | | | |
|---------------------------|---------------------------|--------------------------------------|----------------|------------------|---------------|
| POWERS | | Phase A | Phase B | Phase C | Total |
| Active | (P) | 3626.4 | 2880.0 | 2833.0 | 9339.4 |
| Reactive | (Q) | 317.3 | 2146.0 | 2112.0 | 4575.3 |
| Distortion | (D) | 0.0 | 1102.6 | 1784.5 | 2887.1 |
| Apparent | (U) | 3640 | 3757 | 3959 | |
| PHASOR | (S) | (VA)_{Total} = 10,400 | | PF = 89.8 | |
| APPARENT | (U) | (VA)_{Total} = 10,793 | | PF = 86.5 | |
| ARITH. | (U_{arth}) | (VA)_{Total} = 11,356 | | PF = 82.2 | |



- **Which “kVA” calculation method is correct?**
 - They all are “correct”, by definition.
 - Each utility needs to decide which value is appropriate for their own needs.
 - Phasor Power is what results from calculations based on traditional kWh and kvarh meter readings, using a Phase-Shifting Transformer.
 - Apparent Power provides more complete picture of “cost of service”, expected answers under all conditions.
 - Arithmetic Apparent Power may provide unexpected results (low PF, high kVA) for asymmetrical or unbalanced conditions.



PHASE "X" FORMULAE

| | | |
|---------------------------|---|------------------------------|
| <i>RMS Potential,</i> | $E_X = \sqrt{\sum_{h=1}^H E_{Xh}^2}$ | (Volts) |
| <i>RMS Current,</i> | $I_X = \sqrt{\sum_{h=1}^H I_{Xh}^2}$ | (Amperes) |
| <i>Apparent Power,</i> | $U_X = E_X I_X$ | (kVA) |
| <i>Active Power,</i> | $P_X = \sum_{h=1}^H E_{Xh} I_{Xh} \cos(\alpha_{Xh} - \beta_{Xh})$ | (kW) |
| <i>Re active Power,</i> | $Q_X = \sum_{h=1}^H E_{Xh} I_{Xh} \sin(\alpha_{Xh} - \beta_{Xh})$ | (k var) |
| <i>Distortion Power,</i> | $D_X = \pm \sqrt{U_X^2 - P_X^2 - Q_X^2}$ | (kVA) |
| <i>Phasor Power,</i> | $S_X = +\sqrt{P_X^2 + Q_X^2}$ | (kVA) |
| <i>Fictitious Power,</i> | $F_X = +\sqrt{U_X^2 - P_X^2}$ | (kVA) (a.k.a. "Fuzzy var s") |
| <i>Nonreactive Power,</i> | $N_X = +\sqrt{U_X^2 - Q_X^2}$ | (kVA) |


E_{Xh} and I_{Xh} are the RMS voltage and amperage of harmonic h. α_{Xh} and β_{Xh} are the phase angles of the voltage and current of harmonic h with respect to the reference time-frame. H is the highest harmonic ordinal.




TESCO METERING

DIFFERENT METERS


Aclara kV2c Meter

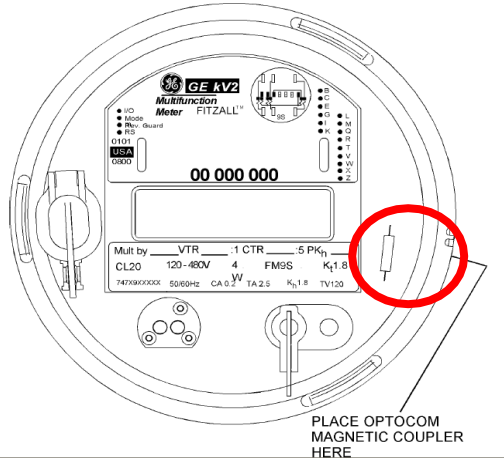

Honeywell A3

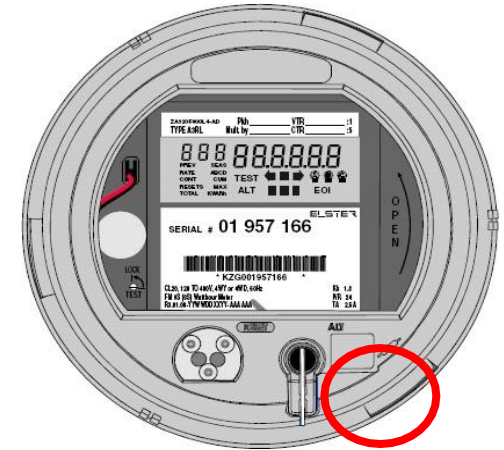

Landis + Gyr S4e

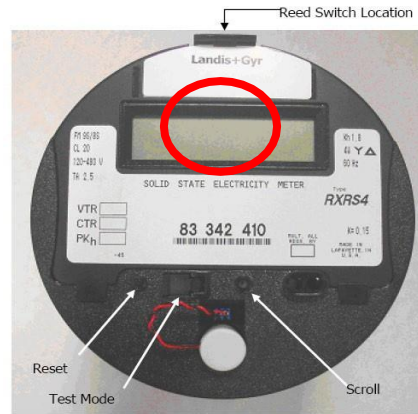

Sensus Icon APX



Itron Sentinel





TESCO METERING


STEP 1: DRAW DIAGRAM FOR...

Power

Meter

Load

Transformer

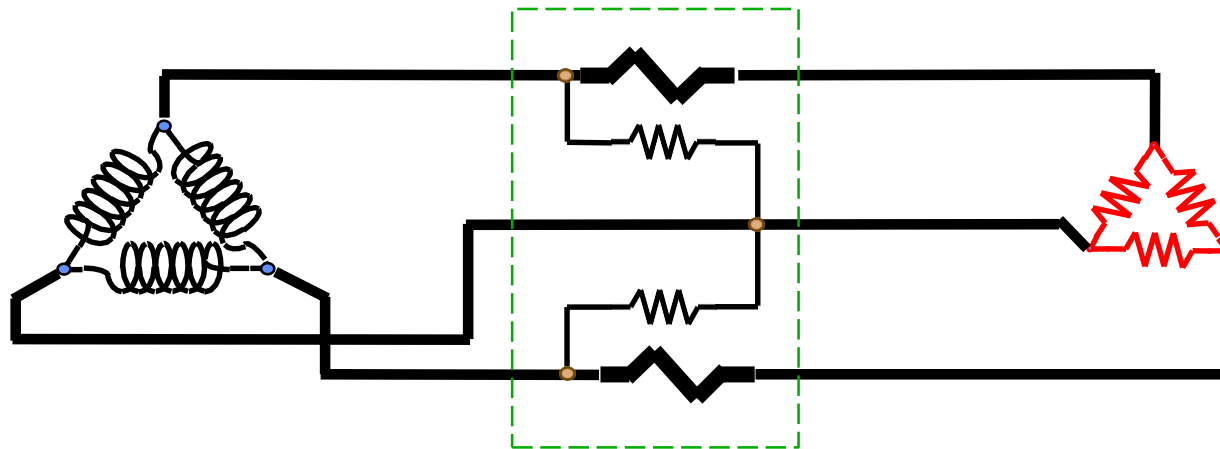

Phasor Construction


STEP 2: DRAW DIAGRAM FOR...

Power

Meter

Load

Transformer

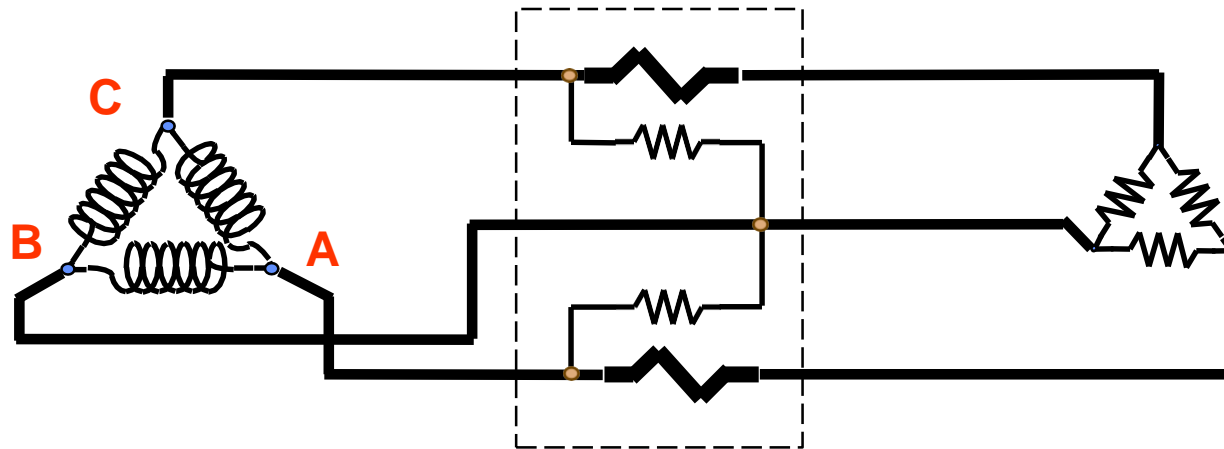

Step 2: Label points of Power Transformer

Phasor Construction



TESCO METERING


STEP 3: DRAW AND LABEL ALL LINE CURRENTS

Power

Meter

Load

Transformer

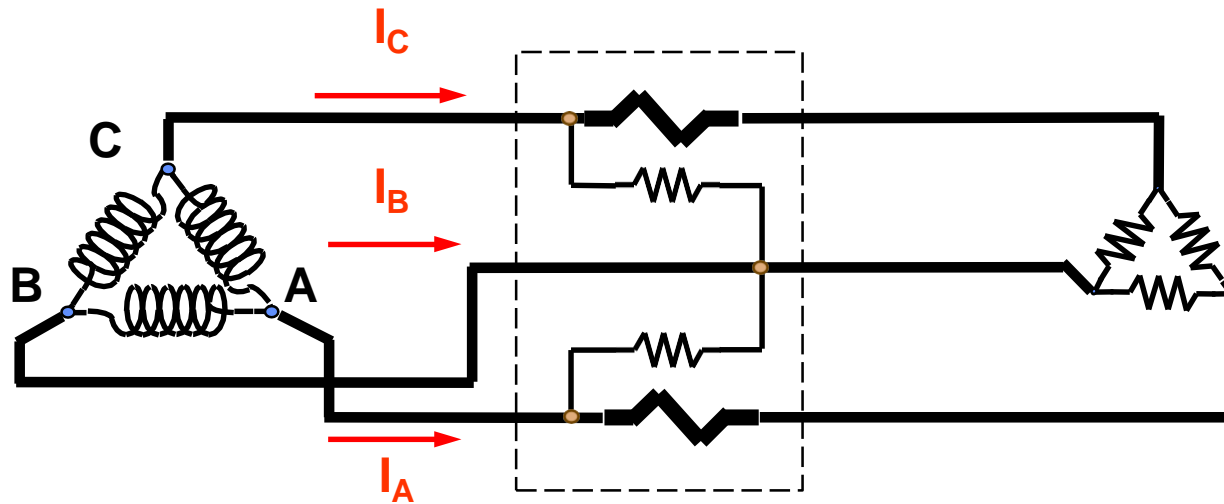

Draw line currents between power transformer and meter. Use arrows with closed points (\longrightarrow). Assume all currents flow from transformer to load. Where necessary, draw power transformer coil currents and label with double subscript notation (I_{BA} , I_{AC} , etc.

Phasor Construction


STEP 4: MARK POLARITY ON ALL CURRENT COILS

Power

Meter

Load

Transformer

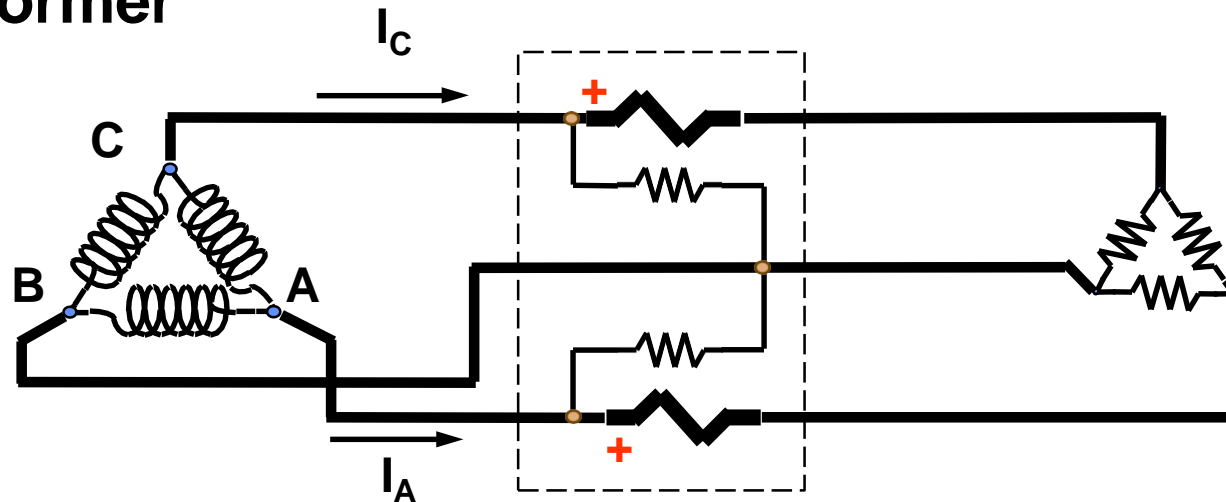

The polarity mark (+) goes on the line side of all current coils except:

- (a): For 2 1/2 stator Z-coil meters. The polarity “+” goes on the load side of the Z-coil.
- (b): For 3-wire, 1-phase meters and the 3-wire stator on the left side of a 4-wire delta meter, the “+” goes on the load side of the right hand coil of the single stator meter, and the “inside” coil of the left hand stator in the 4-wire delta meter.

Phasor Construction


STEP 4: POLARITY OF CURRENT COILS (CONT.)

Power

Meter

Load

Transformer

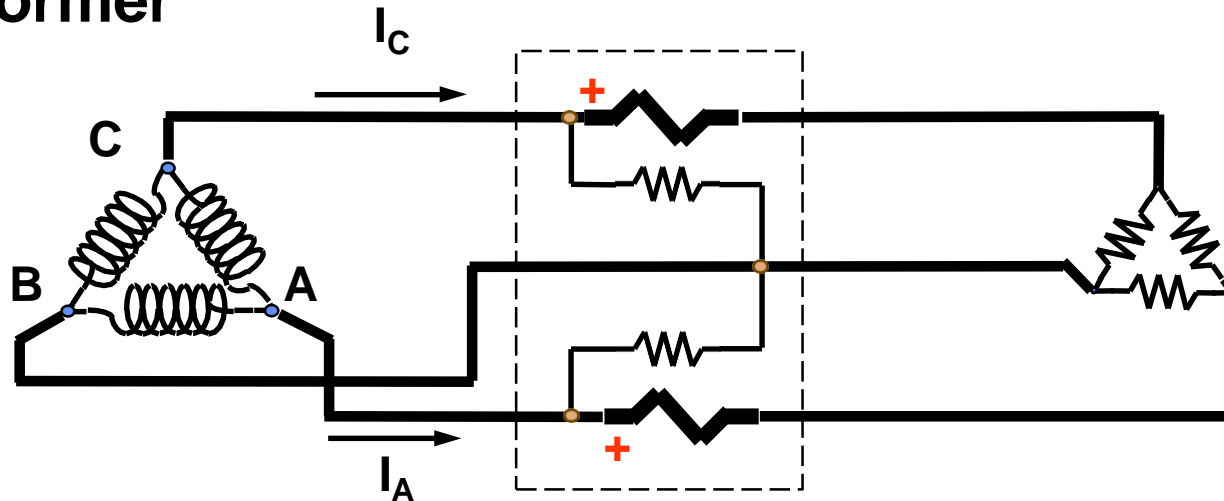

If line current enters the “+” end of a current coil, the coil current is assumed to be in phase with the line current. If, however, the current enters the unmarked end of the coil, the current is assumed to be 180° out of phase with the line current.

Phasor Construction



TESCO METERING


STEP 5: MARK POLARITY ON ALL VOLTAGE COILS

Power

Meter

Load

Transformer

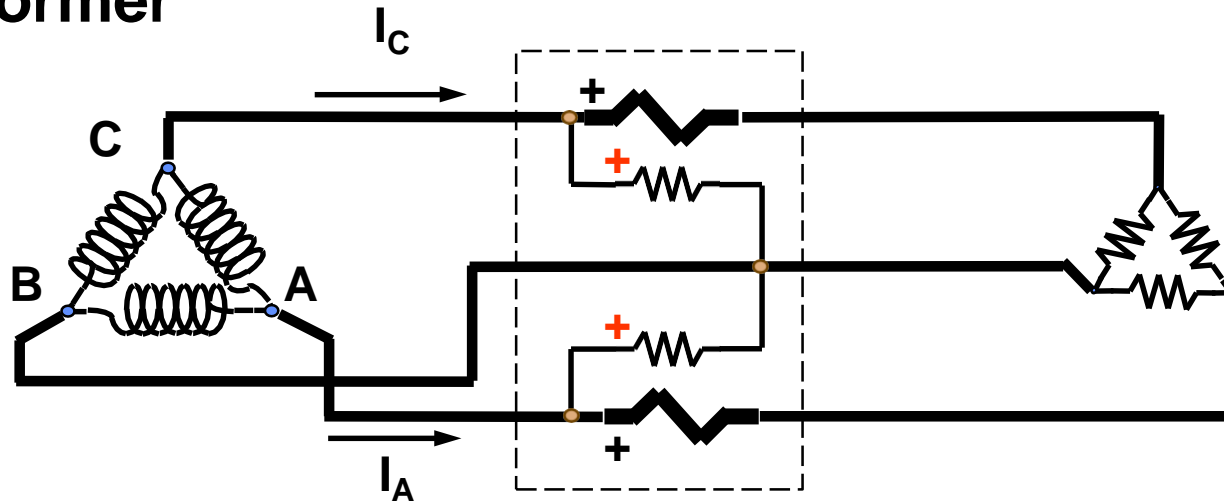

The polarity mark (+) goes on the end of the voltage coil that connects to the “+” end of the current coil.


Phasor Construction

STEP 6: DRAW VOLTAGE ARROWS AT POWER TRANSFORMER

Power Transformer

Meter

Load

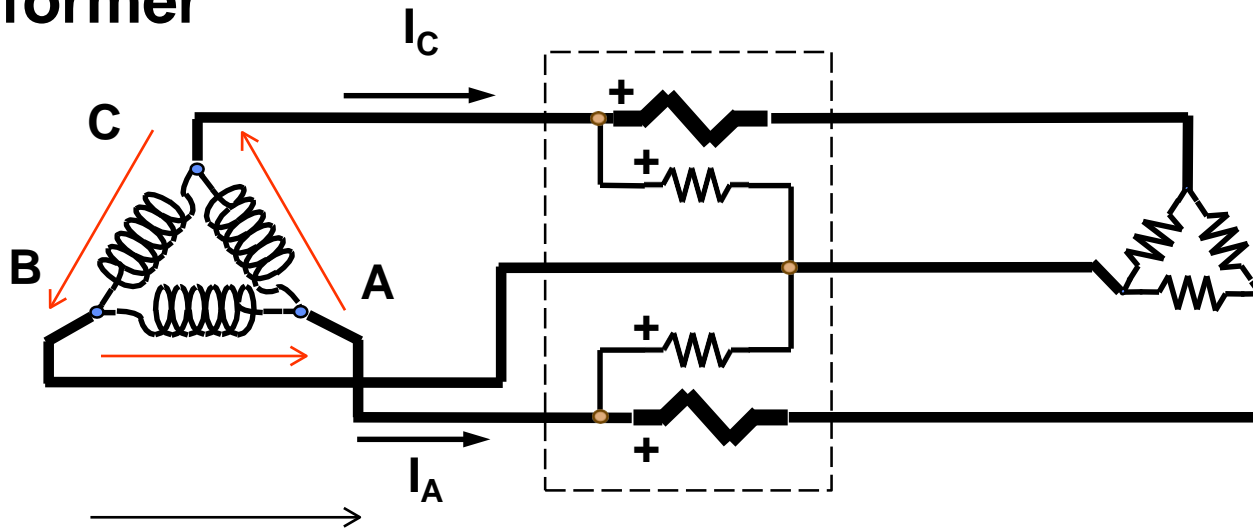


Draw open ended arrows to represent voltage at the power transformer.

- Wye-connected: point away from the neutral.
- Delta-connected: tracing tail-to-head-to-tail, etc., around the delta following a counter-clockwise direction.

Phasor Construction

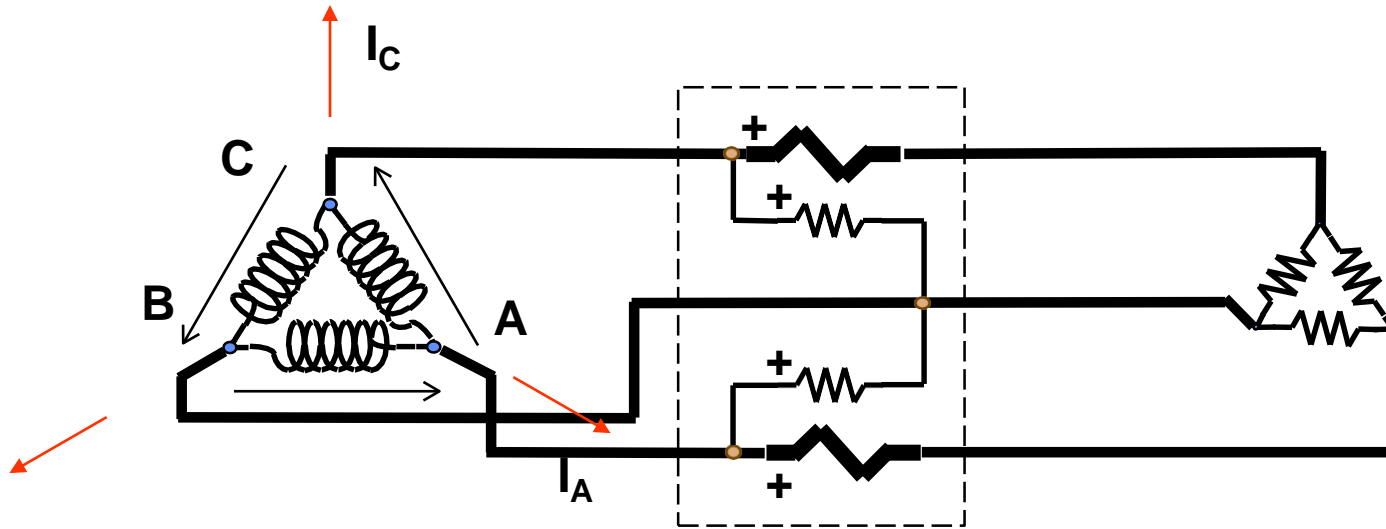STEP 7: ESTABLISH VOLTAGE & CURRENT RELATIONSHIPS



Use Kirchoff's Laws to establish the needed relationships between voltages and currents at the power transformer.

Phasor Construction


STEP 8: COMPLETE THE "SOURCE" PHASORS

Power

Meter

Load

Transformer

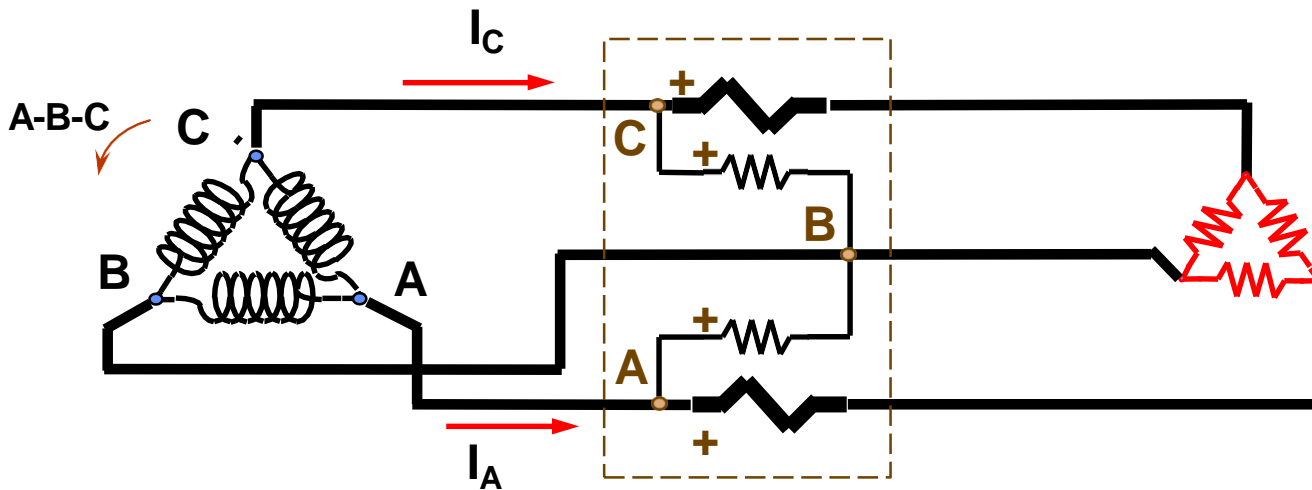

Complete the phasor diagram for the power transformer (source).

Phasor Construction



TESCO METERING


STEP 8: COMPLETE THE "SOURCE" PHASORS

Power


Meter

Load

Transformer

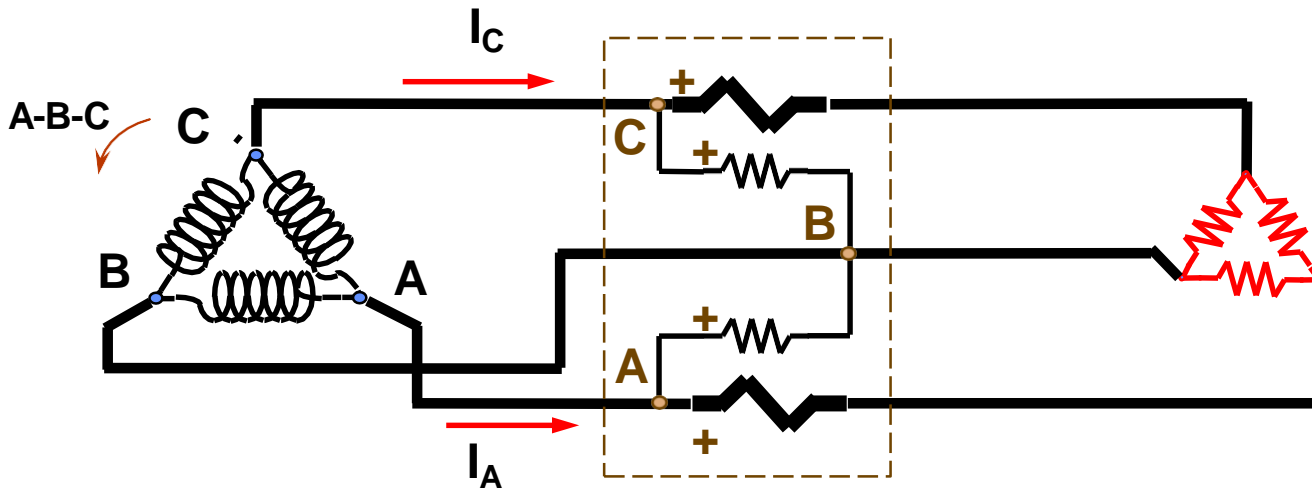

Phasor Construction

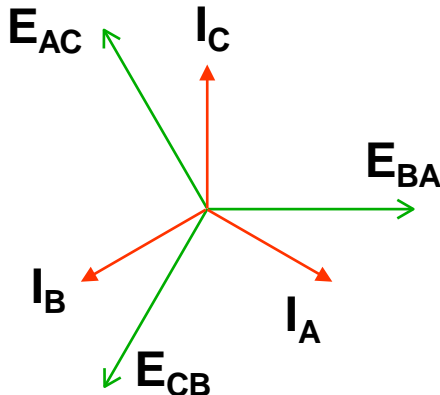


STEP 9: CONSTRUCT METER VOLTAGE PHASORS

Power

Meter

Load

Transformer

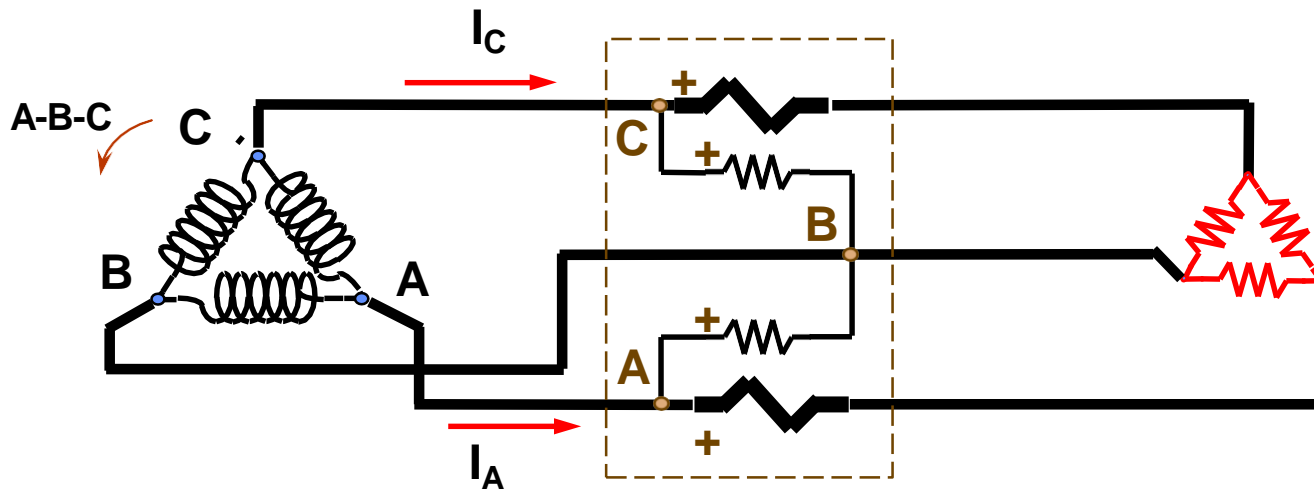

Draw the voltage phasors for the meter, using the tracing method.

Starting at the polarity end of the voltage coil, trace through the voltage coil, back through the source, and return to the polarity end of the voltage coil.

The direction of the METER phasor is the direction traveled through the source transformer.

Phasor Construction



TESCO METERING


STEP 9: CONSTRUCT METER VOLTAGE PHASORS

Power


Meter

Load

Transformer

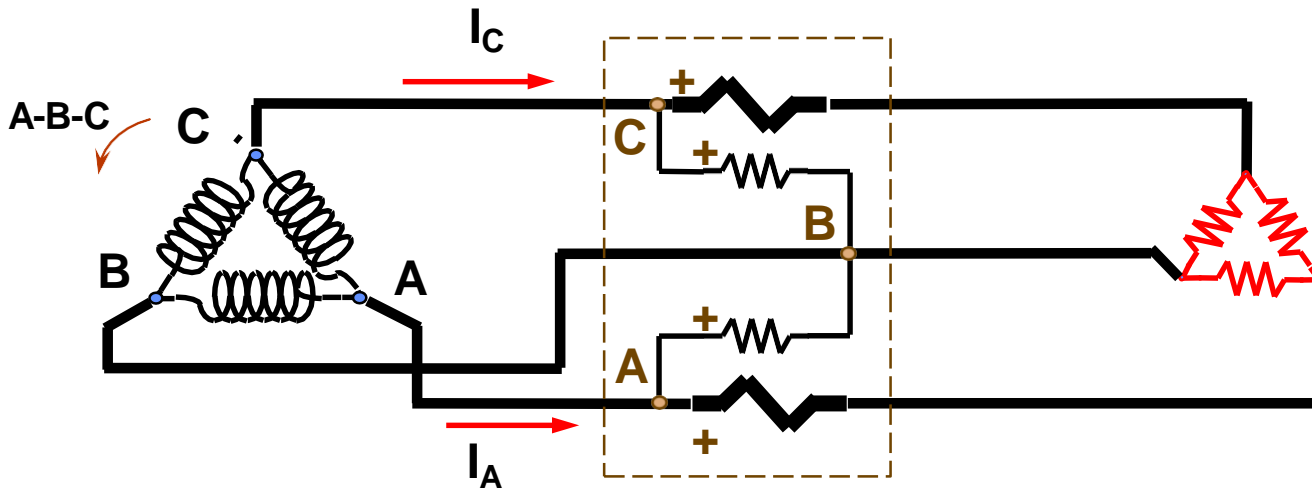

Phasor Construction

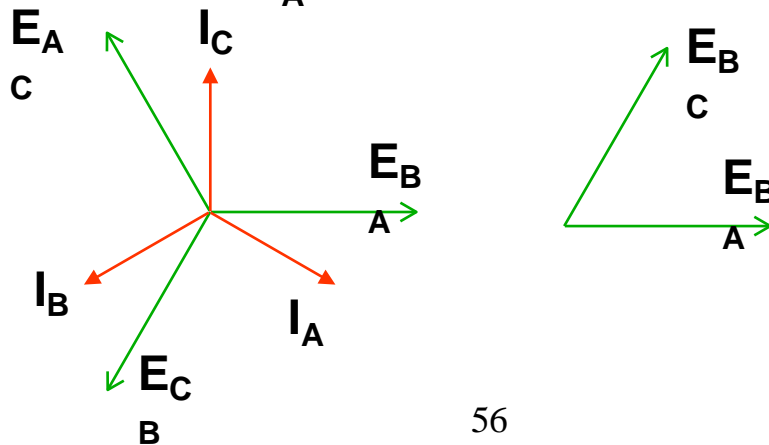


STEP 10: CONSTRUCT METER CURRENT PHASORS

Power

Meter

Load

Transformer

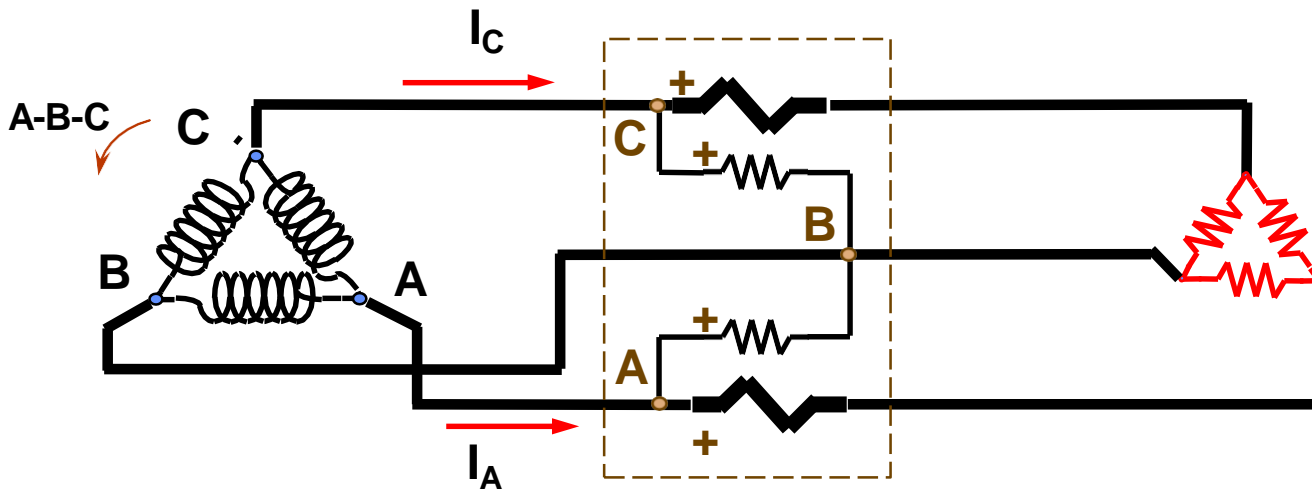

Add meter current phasors by using the relationships developed in step 8, and observing the polarity marks of the current coils. Make sure all voltage and current phasors are labeled, and show the interactions between voltages and currents in the meter stators by connecting the appropriate phasors with elongated ellipses.

Phasor Construction



TESCO METERING


STEP 10: CONSTRUCT METER CURRENT PHASORS

Power Transformer

Meter

Load

Transformer

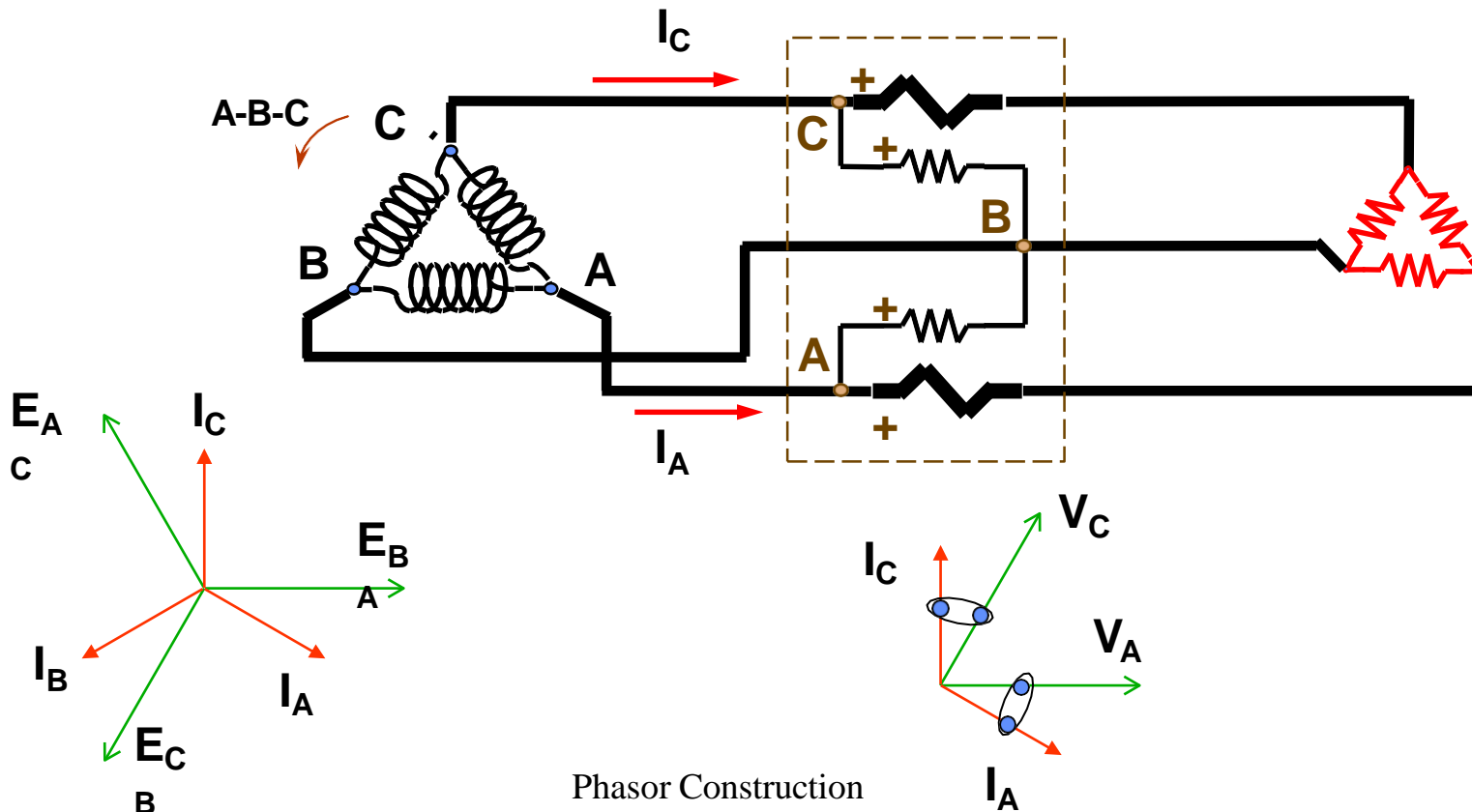


STEP 11: WRITE EQUATION FOR METER WATTS

Power

Meter


Load

Transformer

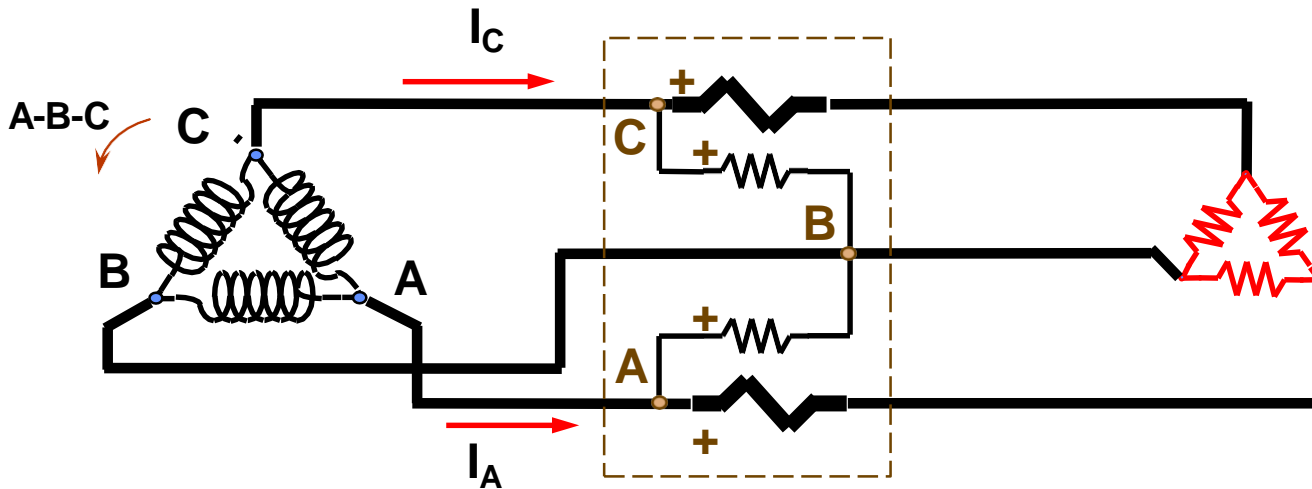

Show the expression for the Meter Watts.

Phasor Construction

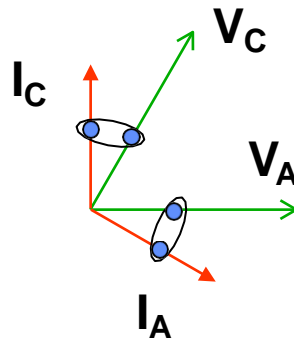


STEP 11: WRITE EQUATION FOR METER WATTS

Power

Meter

Load


Transformer

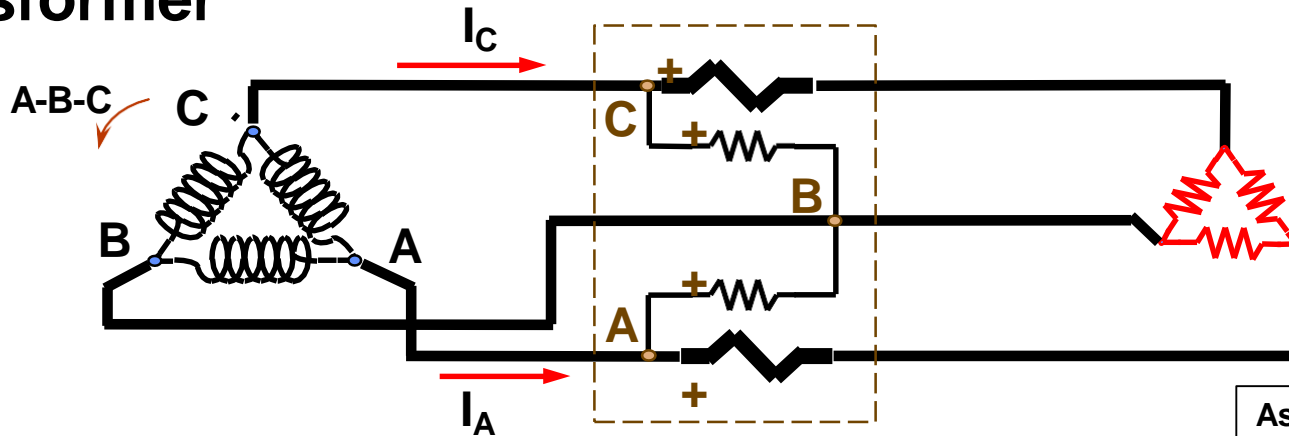

Show the expression for the Meter Watts.

Assuming balanced 3-phase load and balanced voltages

$$\begin{aligned}
 \text{MeterWatts} &= V_A I_A \cos(30 + \theta_A) + V_C I_C \cos(30 - \theta_C) \\
 &= V_{LL} I_L \cos(30 + \theta) + V_{LL} I_L \cos(30 - \theta) \\
 &= V_{LL} I_L [(\cos 30 \cos \theta - \sin 30 \sin \theta) + (\cos 30 \cos \theta + \sin 30 \sin \theta)] \\
 &= V_{LL} I_L \left[\left| \left(\frac{\sqrt{3}}{2} \cos \theta \right) \right| + \left| \left(\frac{\sqrt{3}}{2} \cos \theta \right) \right| \right] \\
 &= \sqrt{3} V_{LL} I_L \cos \theta
 \end{aligned}$$

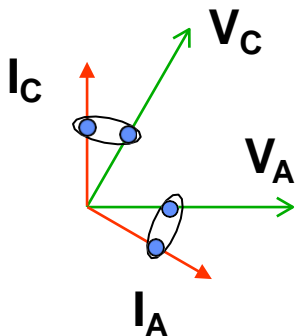


STEP 12: WRITE EQUATION FOR LOAD WATTS

Power

Meter

Load

Transformer

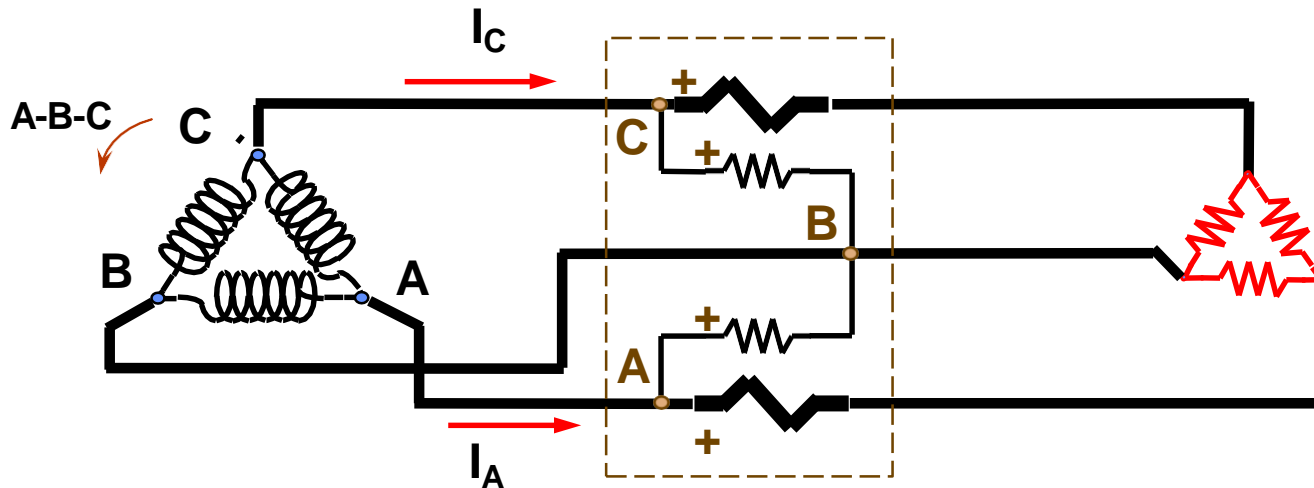

Show the expression for the Delivered Watts, or Load Watts.

Phasor Construction


STEP 12: WRITE EQUATION FOR LOAD WATTS

Power

Meter

Load

Transformer

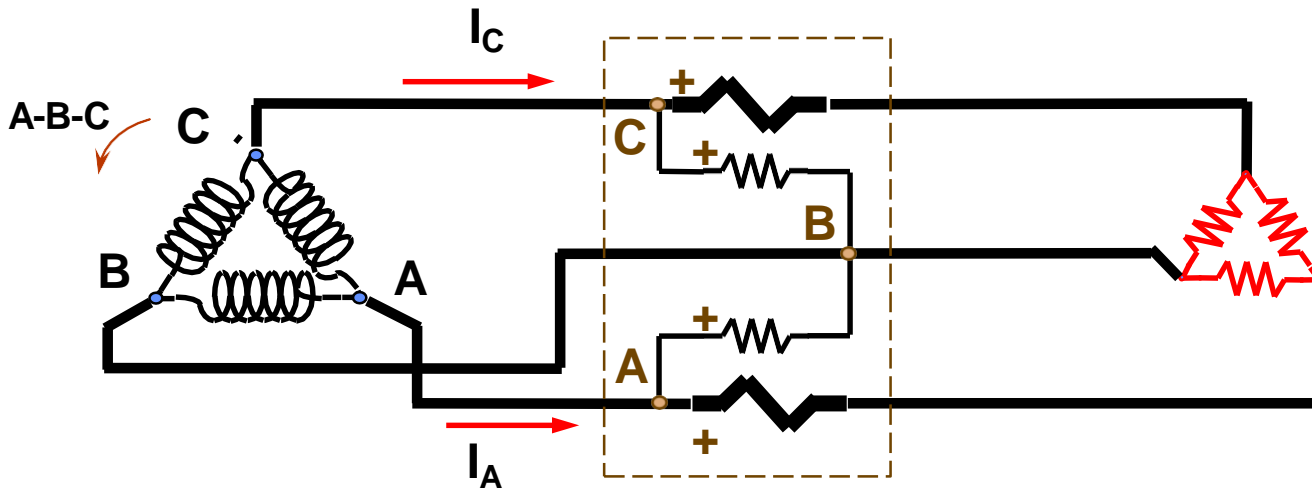

Show the expression for the Delivered Watts, or Load Watts.

For a balanced 3-phase load:

$$\text{Load Watts} = \sqrt{3} V_{LL} I_L \cos(\theta)$$

Phasor Construction


STEP 13: CALCULATE "PERCENT REGISTRATION"

Power

Meter

Load

Transformer

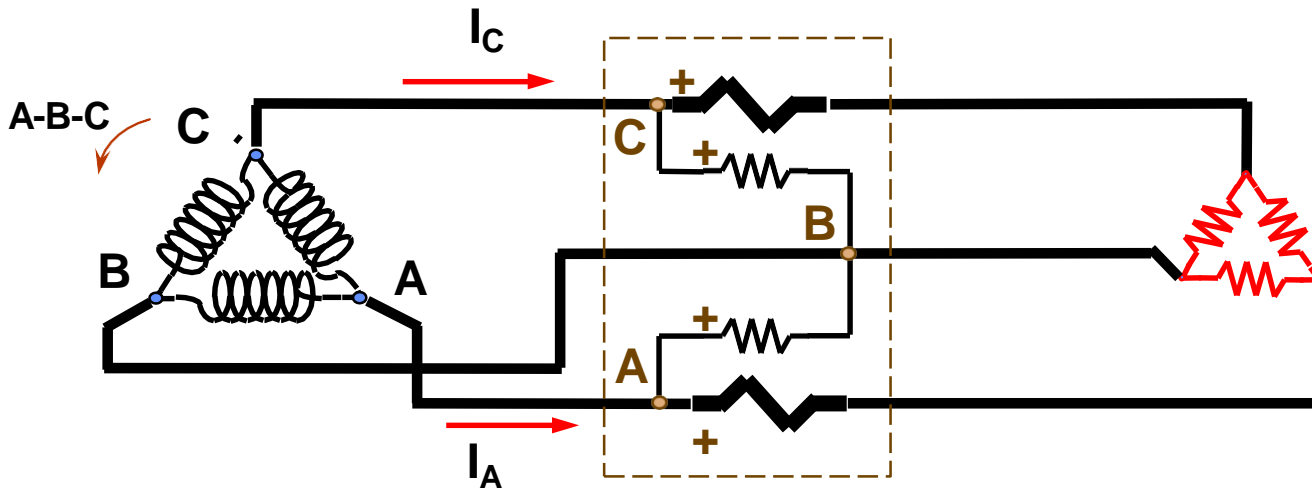

Calculate the percent registration of the meter by dividing the Meter Watts by the Load Watts, then multiplying the result by 100%.

Phasor Construction



TESCO METERING


STEP 13: CALCULATE "PERCENT REGISTRATION"

Power

Meter

Load

Transformer

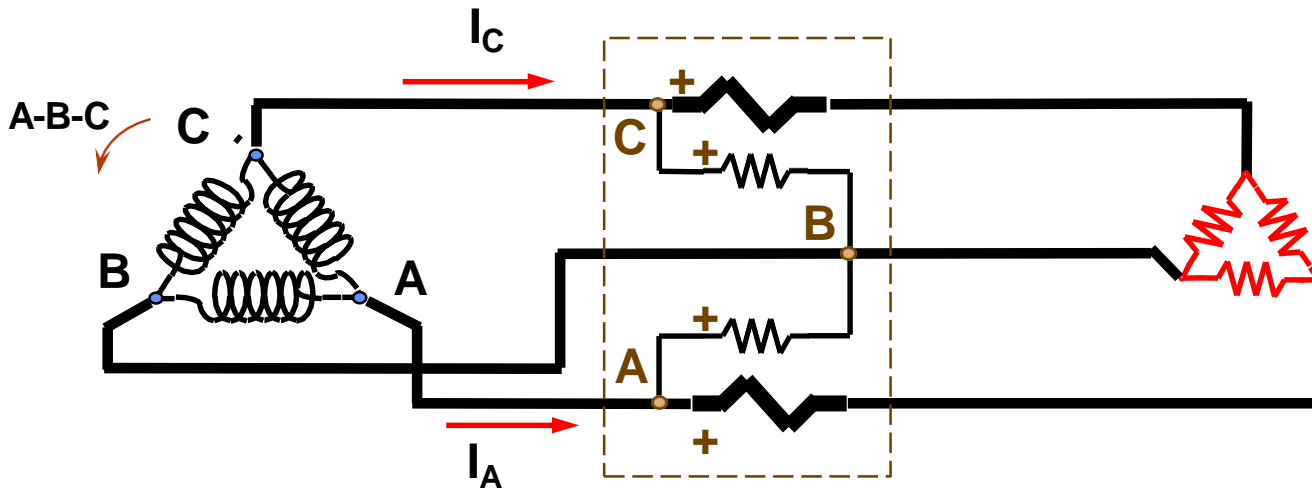

Calculate the percent registration of the meter by dividing the Meter Watts by the Load Watts, then multiplying the result by 100%.

$$\text{Percent Registration} = \frac{\text{Meter Watts}}{\text{Load Watts}} \times 100\%$$

Phasor Construction

$$= \frac{\sqrt{3} V_{LL} I_L \cos \theta}{\sqrt{3} V_{LL} I_L \cos \theta} \times 100\%$$

$$= 100\%$$



TESCO METERING

QUESTIONS AND DISCUSSION

Perry Lawton

Northeastern Regional Sales Manager

perry.lawton@tescometering.com



TESCO Metering *Bristol, PA*

215.500.7511

This presentation can also be found under Meter Conferences and Schools on the TESCO website: tescometering.com

ISO 9001:2015 Certified Quality Company
ISO 17025:2017 Accredited Laboratory



TESCO METERING

TESCO HOSPITALITY SUITE

You're invited...


We would like you to join us in the TESCO Hospitality Suite for networking and more discussions about metering. The discussion will not be exclusively metering.....but we love metering and that is the most common topic.

TESCO Hospitality Suite – Brighton Tower

Monday and Tuesday 8:00 PM – 10:00 PM



We Hope you Can Join Us!

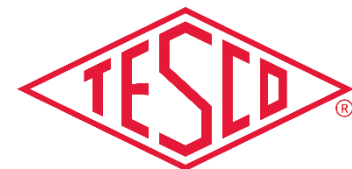

TESCO METERING